

## **EXPERIMENT NO. 2**

### **APPLICATIONS OF LOGIC GATES AND K-MAP**

**NAME:** \_\_\_\_\_ **; ID:** \_\_\_\_\_ **;**

**GROUP NO.:** \_\_\_\_\_ **; DATE** \_\_\_\_\_ **.**

#### **Learning Outcomes**

1. Use a Karnaugh map to simplify the expression.
2. Build and test logic that implements the simplified expression for following applications
  - a. Addition of two bits
  - b. 4-bit Gray to Binary Code conversion
  - c. Invalid BCD code detector
  - d. Select one of the two inputs and pass it to output.
  - e. Compare two bits

#### **Equipments and components Required**

Analog/Digital IC tester, Power Supply, Bread Board, LED Panel, Panel of toggle switches, Digital Multi Meter (DMM).

7408 – Quad 2-input AND

7432 – Quad 2-input OR

7486 – Quad 2-input XOR

7404 \_ Quad 1-input NOT

#### **Experiment:**

**Verify following parameters and complete the checklist before circuit implementation.**

S.No.	Description	Remark (√ OR ×)
1	Check DC voltage from power supply using Multimeter.	
2	Is proper voltage range of DC power supply selected?	
3	Are all switches and LEDs working?	
4	Are all ICs tested using IC tester?	
5	Are required ICs placed correctly on bread board?	
6	Identified pin no.1 of IC?	
6	Do you know Logical function and pin configuration of all ICs? (Refer Data sheets)	
7	DC power supply is OFF till you complete the connections.	
8	All the truth tables with theoretically calculated values and required circuit diagrams are complete?	

**Run 01#:** Following truth table as Table 2.1 shows output of a logical circuit that adds two binary bits. The circuit is known as Half Adder. The circuit has two inputs and two outputs S (SUM) and C (CARRY). Derive logical expression for S And C from the given truth table in SOP form. Build and test logic that implements the simplified expression.

**Include Pin numbers of each logic gate on the drawing.**

i/p		o/p		Logic For 'S'	Observed output (S)	o/p		Logic for 'C'	Observed Output (C)
A	B	S	C						
0	0	0				0			
0	1	1				0			
1	0	1				0			
1	1	0				1			
Logical Expression (SOP form) for 'S' =									
Logical Expression (SOP form) for 'C' =									



Table 2.1: Truth Table for Half Adder

Fig 2.1: Circuit Diagram for Half Adder

**Run #02:** As an application of XOR gates, we would be implementing a circuit for converting a 4-bit gray code to its equivalent binary number. Given a 4 bit gray code  $G_3G_2G_1G_0$  its equivalent binary number given by:

$B_3 = \dots$                        $B_2 = \dots\dots\dots$                        $B_1 = \dots\dots\dots$                        $B_0 = \dots\dots\dots$

Draw circuit diagram as Fig 2.2. **Include Pin numbers of each logic gate on the drawing.**

 


Fig 2.2: Gray to Binary code converter

Note down your observations in following truth table as Table 2.2.

$G_3G_2G_1G_0$	$B_3B_2B_1B_0$ (output )	$B_3B_2B_1B_0$ (Observed Output)	$G_3G_2G_1G_0$	$B_3B_2B_1B_0$ (output )	$B_3B_2B_1B_0$ (Observed Output)
00000			1100		
0001			1101		
0011			1111		
0010			1110		
0110			1010		
0111			1011		
0101			1001		
0100			1000		

Table 2.2: Truth Table for Gray to Binary code conversion

**Run 03 #:** Implement a logic circuit to act as a invalid BCD code detector using Logic Gates. Complete the truth table shown as Table 2.3 with your observations.

Decimal equivalent	B3	B2	B1	B0	Valid BCD	Invalid BCD	Observed output
0	0	0	0	0	1	0	
1	0	0	0	1	1	0	
2	0	0	1	0	1	0	
3	0	0	1	1	1	0	
4	0	1	0	0	1	0	
5	0	1	0	1	1	0	
6	0	1	1	0	1	0	
7	0	1	1	1	1	0	
8	1	0	0	0	1	0	
9	1	0	0	1	1	0	
10	1	0	1	0	0	1	
11	1	0	1	1	0	1	
12	1	1	0	0	0	1	
13	1	1	0	1	0	1	
14	1	1	1	0	0	1	
15	1	1	1	1	0	1	

Table 2.3: Truth Table for Invalid BCD code detector

(a) Complete and use K-map shown as Figure 2.3 to simplify boolean expression for the invalid codes. Draw the circuit diagram as Fig 2.4, space given below.

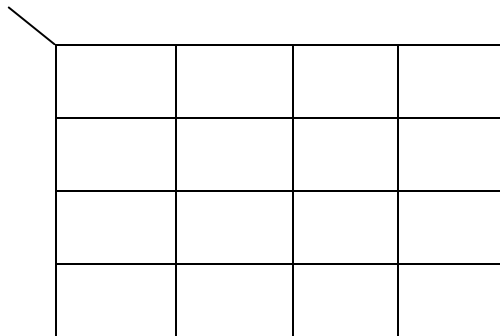



Fig2.3: k-map for invalid BCD code detector

Simplified logical Expression for Invalid BCD code detector circuit:=

---



---



---



---



---



Fig 2.4: Circuit Diagram for invalid BCD code detector

**Run 04 #:** Following truth table as in Table 2.4 shows output of a logical circuit which selects one of the two inputs and pass it to output. The circuit is called as a 2:1 Multiplexer (MUX). Complete K-map shown as Figure 2.5 and use it to simplify logical expression for 2:1 MUX. Draw the circuit diagram as Fig 2.6, space given below.

Input			o/p Z	Z (Observed output)
A1	A0	S		
0	0	0	0	
0	0	1	0	
0	1	0	1	
0	1	1	0	
1	0	0	0	
1	0	1	1	
1	1	0	1	
1	1	1	1	

Fig 2.5:K-map for 2:1 MUX




Table 2.4: Truth Table for 2:1 MUX;

Fig 2.6: Circuit diagram for 2:1 MUX

Implement the circuit and record your observations as observed output in Table 2.4

**Run 05 #:** Following truth table as in Table 2.5 shows output of a logical circuit which compare two bits .... The circuit is called as a 1 bit comparator. Complete K-map shown as Figure 2.7 and simplify logical expression. Draw the circuit diagram as Fig 2.8. Record your observations in Table 2.6

Input		A>B	A>B (Observed output)	A<B	A<B (Observed output)	A=B	A=B (Observed output)
A	B						
0	0	0		0		1	
0	1	0		1		0	
1	0	1		0		0	
1	1	0		0		1	

Table 2.5: Truth Table for 1 bit comparator


Fig 2.7: K-map for 1 bit comparator



Fig 2.8: Circuit Diagram for 1 bit comparator