



IS C351

Computer Architecture & Organization

Lab

Week #1

Getting Started With Verilog

Getting Started With Verilog



Motivation

Introduction to Verilog

First Verilog Program

Testing Verilog Program

Styles of Coding

Structural Coding



Getting Started With Verilog

Motivation

Introduction to Verilog

First Verilog Program


Testing Verilog Program

Styles of Coding

Structural Coding


Motivation

 Scalability - From gates to microprocessors



1971

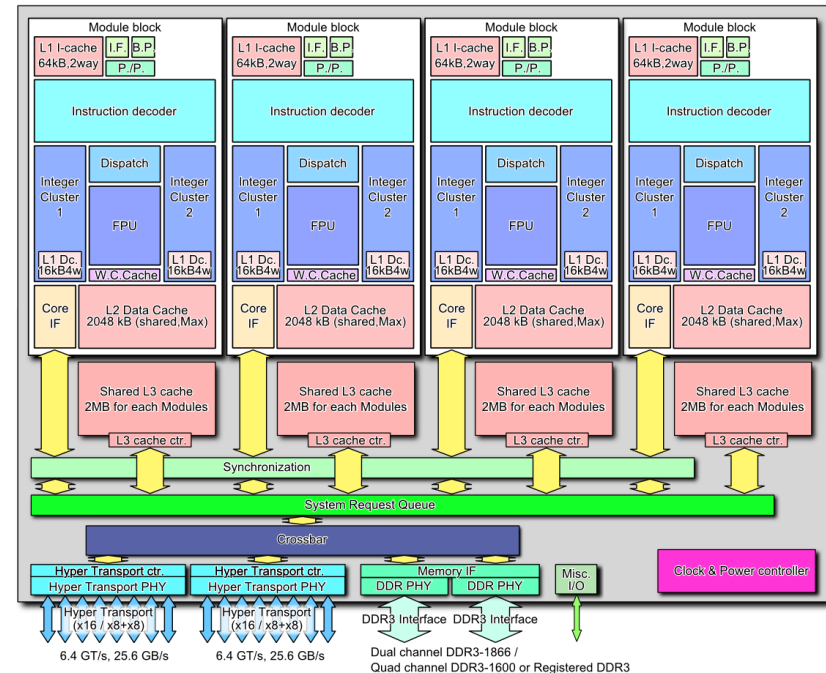Intel 4004 microprocessor
~2,300 transistors @ 1 MHz
Hand-drawn schematic (circuit diagram)
One-man team




2011

AMD Bull Dozer microprocessor
>1.2 Billion transistors @ 1GHz
Hierarchical Block Diagram
> 50 people


Motivation

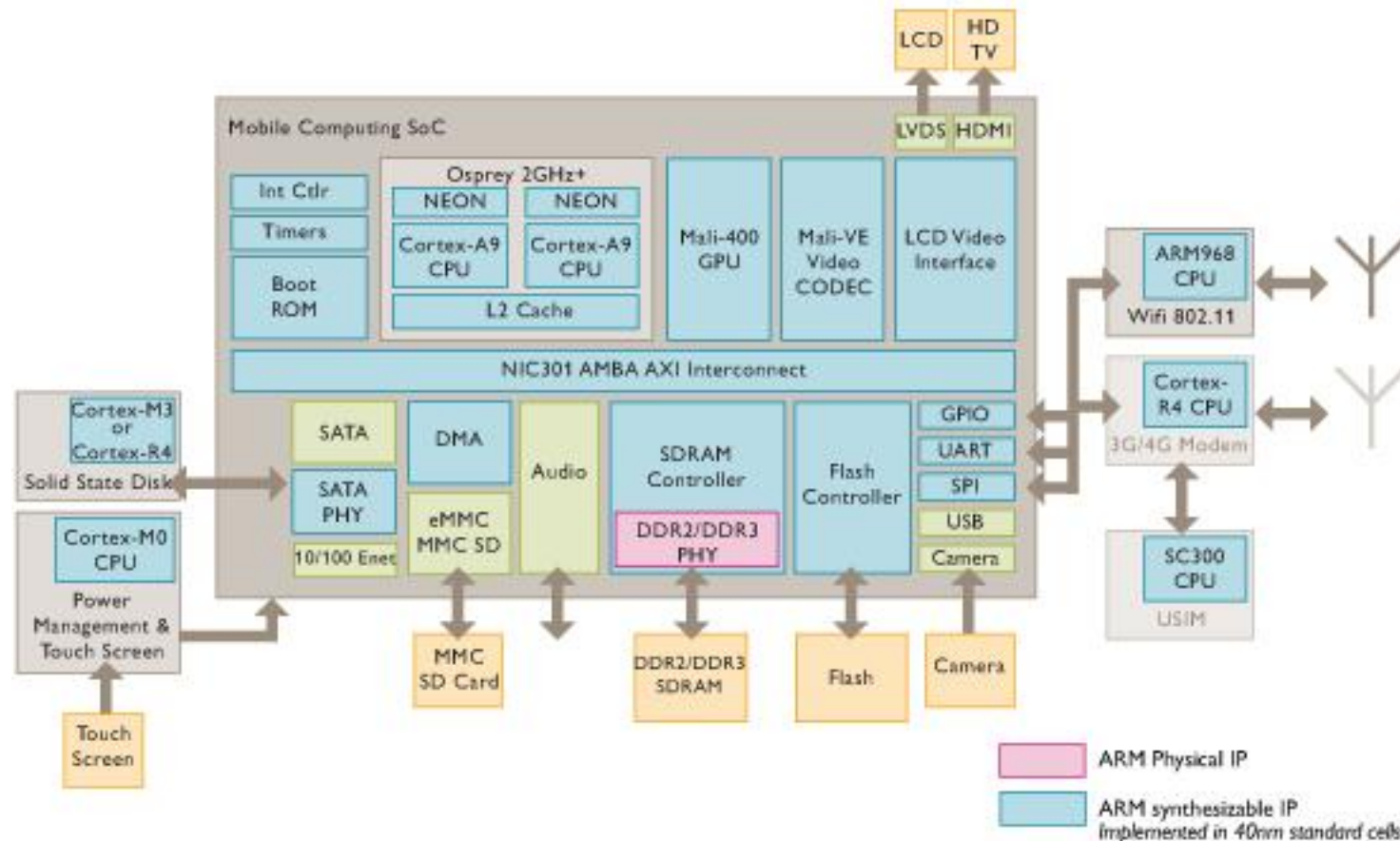Reuse – ARM Processors and related Intellectual Property



Motivation

Rapid Prototyping

 

How does it benefit to you?

Makes hardware development approachable for the software engineers!!



Getting Started With Verilog

Motivation

Introduction to Verilog

First Verilog Program

Testing Verilog Program

Styles of Coding

Structural Coding

Context



Describe the Circuit

HDL
Description

Simulation

Verify the Circuit –
functional, timing and
power constraints

Synthesis

Create the Circuit –
mapping to
implementation platform


Context – Simple Example

HDL Description

```

module mux(y,a,b,sel);
  output reg y;
  input wire a,b,sel;

   always @(*)
  begin
    if (sel)
      y = a;
    else
      y = b;
  end
endmodule
  
```



Synthesis

Simulation





Introduction to Verilog

- Originated at Automated Integrated Design Systems (renamed Gateway) in 1985
- C-like (not C)
- Originally for simulation; synthesis added later.
- Case sensitive, weakly typed language
- New additions to the language – System Verilog and Verilog-AMS



Getting Started With Verilog

Motivation

Introduction to Verilog

First Verilog Program

Testing Verilog Program

Styles of Coding

Structural Coding



Simple AND Gate in Verilog

```
module and_gate(out,in1,in2);  
    output wire out;  
    input wire in1,in2;  
    //use and gate primitive  
    and AND0(out,in1,in2);  
endmodule
```



Keywords in Verilog

module and_gate(out,in1,in2);

output wire out;

input wire in1,in2;

//use and gate primitive

and AND0(out,in1,in2);

endmodule

■ Verilog key words



Module Details in Verilog

```
module and_gate(out,in1,in2);  
    output wire out;  
    input wire in1,in2;  
    //use and gate primitive  
    and AND0(out,in1,in2);  
endmodule
```

module name

ports* with output ports followed by input ports

Component instantiation


port – input / output connection(wire) of a digital circuit



Port Declarations in Verilog

```
module and_gate(out,in1,in2);  
    output wire out; ← output port declaration  
    input wire in1,in2; ← input port declaration  
    //use and gate primitive  
    and AND0(out,in1,in2);  
endmodule
```


Component Instantiation in Verilog

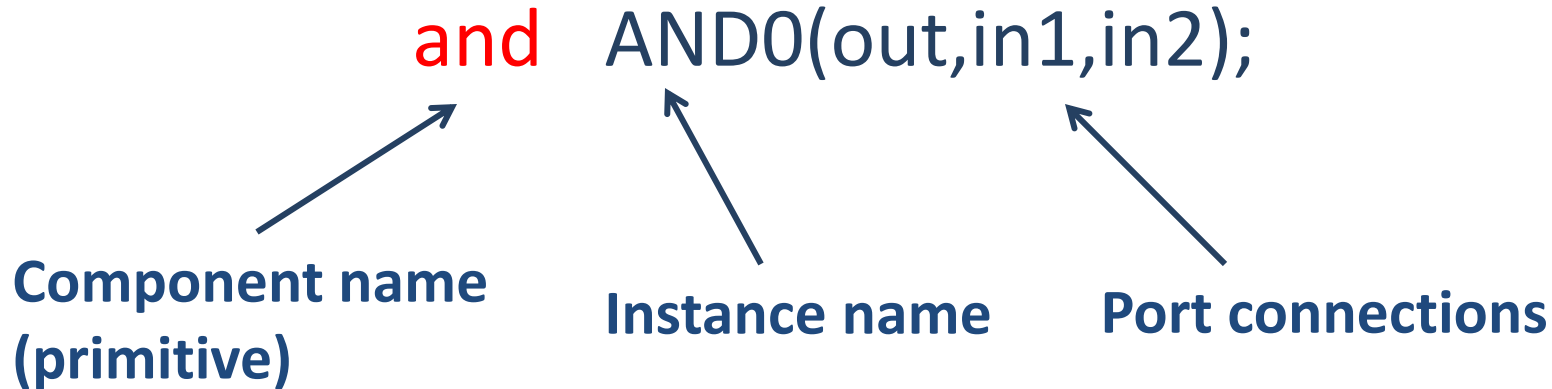

- Primitive – basic component provided by Verilog
- User defined primitives (UDP) are also possible (discussed later)



Semi-colons in Verilog

```
module and_gate(out,in1,in2);
```

```
    output wire out;
```

```
    input wire in1,in2;
```

```
    //use and gate primitive
```

```
    and AND0(out,in1,in2);
```

```
endmodule
```


most statements end
with semi-colon



Comments in Verilog

```
module and_gate(out,in1,in2);  
    output wire out;  
    input wire in1,in2;  
    //use and gate primitive  
    and AND0(out,in1,in2);  
    /*  
    multi-line comment  
    */  
endmodule
```

comments

 



Getting Started With Verilog

Motivation

Introduction to Verilog


First Verilog Program

Testing Verilog Program

Styles of Coding

Structural Coding

Testbench

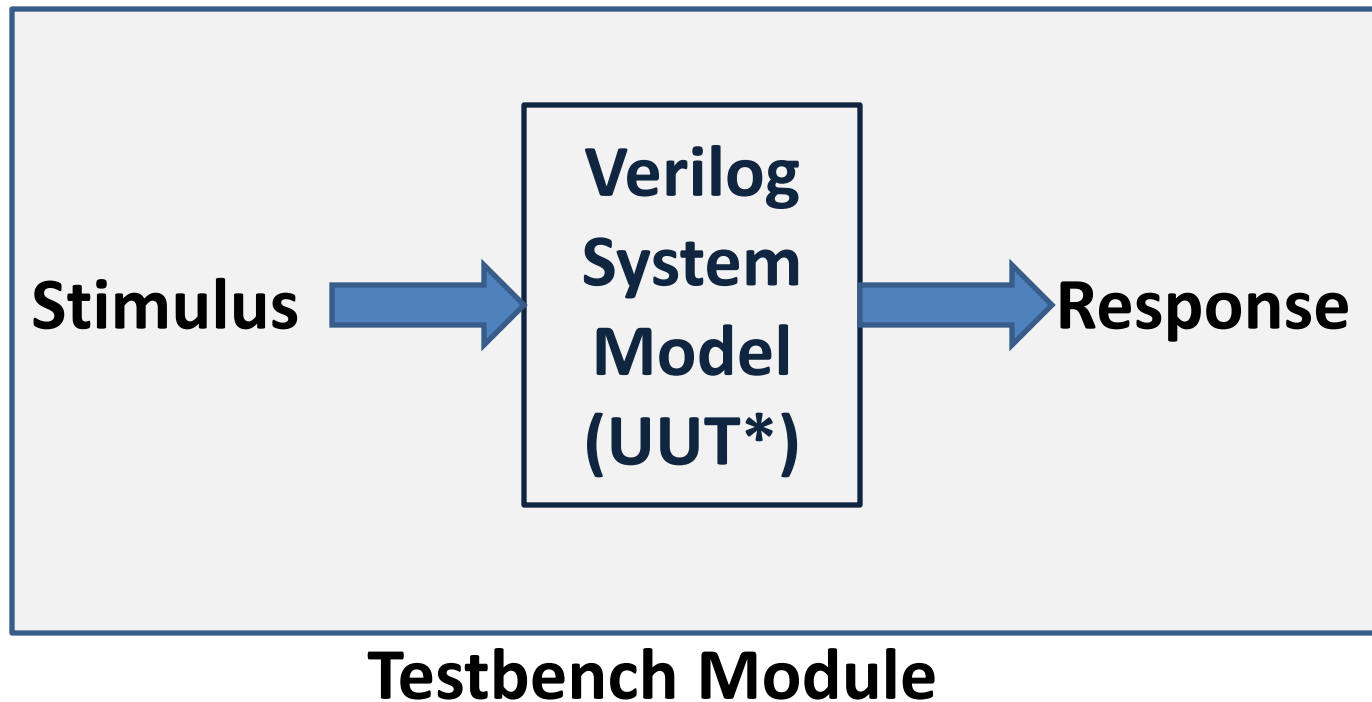

UUT – Unit Under Test



Testbench Structure

```
`timescale 1ns/1ps
```

```
module tb_<foo_module_name> ();
```

```
    //declare all outputs of UUT as wires
```

```
    //declare all inputs of UUT as registers
```

```
    //instantiate the component (UUT – unit under test)
```

```
    //optional block
```

```
    initial
```

```
        begin
```

```
            //initialization code
```

```
        end
```

...continued



Testbench Structure

//optional block

always

begin

//iterative code

end

endmodule



Testbench for AND gate

```
`timescale 1ns/1ps
```

```
module tb_and_gate();
```

```
    wire out;           //all outputs become wires
```

```
    reg in1,in2;        //all inputs become registers
```

```
    and_gate AND0(out,in1,in2);
```

...continued



Testbench for AND gate

//executed at the beginning of simulation

initial

begin

in1 = 1'b0; in2 = 1'b0;

#10 in1 = 1'b0; in2 = 1'b1;

#10 in1 = 1'b1; in2 = 1'b0;

#10 in1 = 1'b1; in2 = 1'b1;

#10 \$stop;

end

system task

endmodule

assignment
delay

Getting Started With Verilog



Motivation

Introduction to Verilog


First Verilog Program

Testing Verilog Program

Styles of Coding

Structural Coding

How Do We Describe a Digital Circuit?

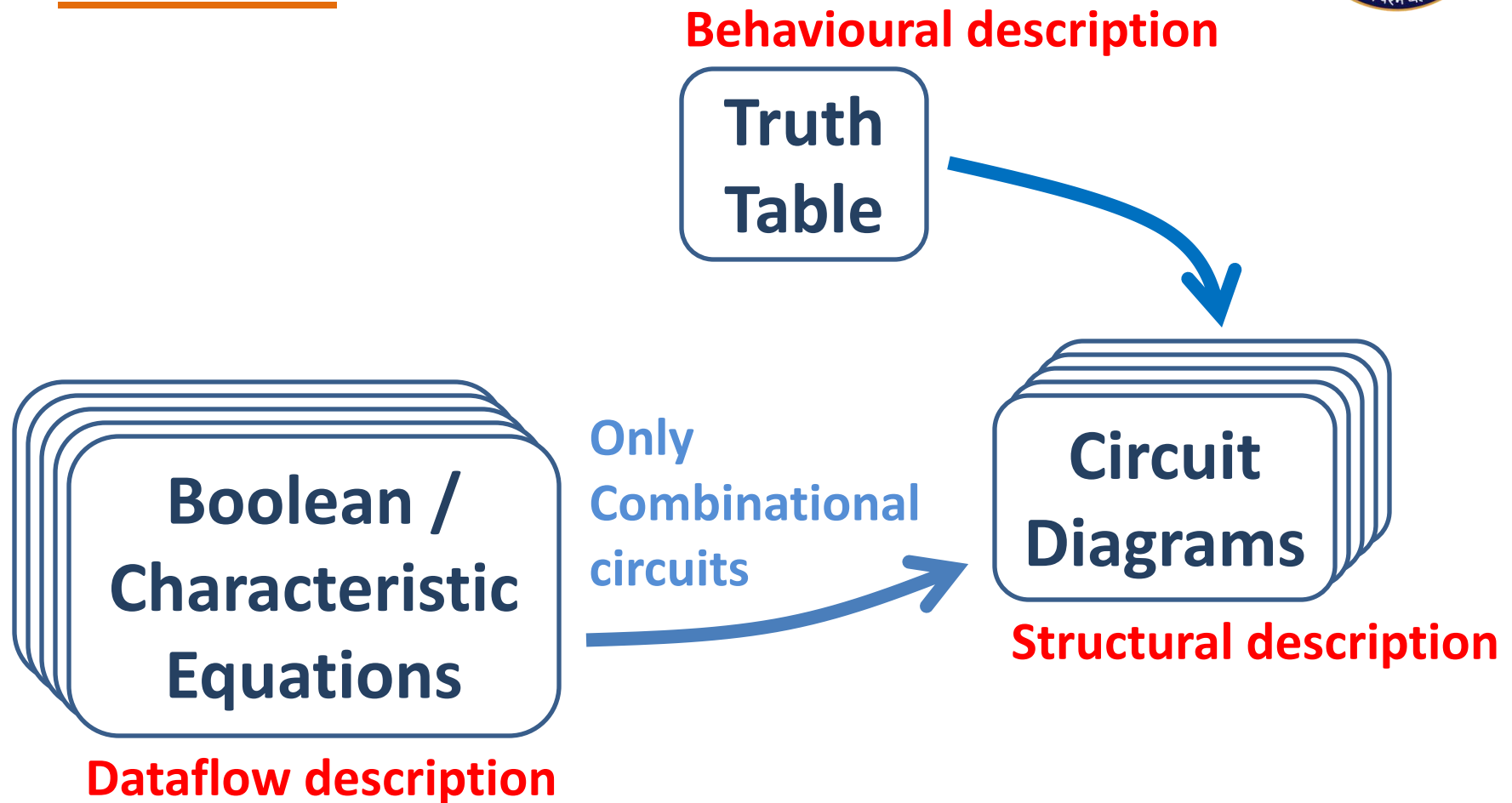



Behavioural Description

- Describe the behaviour (truth-table) of the circuit
- Scalable description
- Synthesizable – Synthesizer generates the circuit automatically
- **Most preferred form for practical designs**

Behavioural Coding Example – Half Adder Circuit



Half Adder Truth Table

a	b	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Behavioural Coding Example – Half Adder Circuit



```
module half_adder (sum, carry, a, b);  
    output reg sum,carry;  
    input wire a,b;  
  
    always @(*)  
        begin
```

...continued

Behavioural Coding Example – Half Adder Circuit



```
casex ({a,b})
```

```
    2'b00:      sum = 1'b0; carry = 1'b0;
```

```
    2'b01:      sum = 1'b1; carry = 1'b0;
```

```
    2'b10:      sum = 1'b1; carry = 1'b0;
```

```
    2'b11:      sum = 1'b0; carry = 1'b1;
```

```
    default:    sum = 1'bx; carry = 1'bx;
```

```
endcase
```

```
end
```

```
endmodule
```




Dataflow Description

- Describe the functionality as boolean equations
- Mostly useful for functional verification
- Not always synthesizable
- Use with caution

Dataflow Coding Example – Half Adder Circuit


 
```
module half_adder (sum, carry, a, b);  
    output wire sum, carry;  
    input wire a, b;  
  
    assign sum = a ^ b;  
    assign carry = a & b;  
  
endmodule
```






Structural Description

- Describe the circuit one module (component) at a time
- One-to-One correspondence with the synthesized circuit
- Useful in hierarchical design
- Very painful
- **What you say is what you get**

Structural Coding Example – Half Adder Circuit


 
```
module half_adder (sum, carry, a, b);  
    output wire sum, carry;  
    input wire a, b;  
  
    xor    XOR0(sum, a, b);  
    and    AND0(carry, a, b);  
  
endmodule
```



One Last Word on Styles



*What's in a name? that which we call a rose
By any other name would smell as sweet;*

- Juliet to Romeo

**Things are different in Verilog;
Coding Style matters to others!!!**



Getting Started With Verilog

Motivation

Introduction to Verilog


First Verilog Program

Testing Verilog Program

Styles of Coding

Structural Coding

Full-Adder Circuit

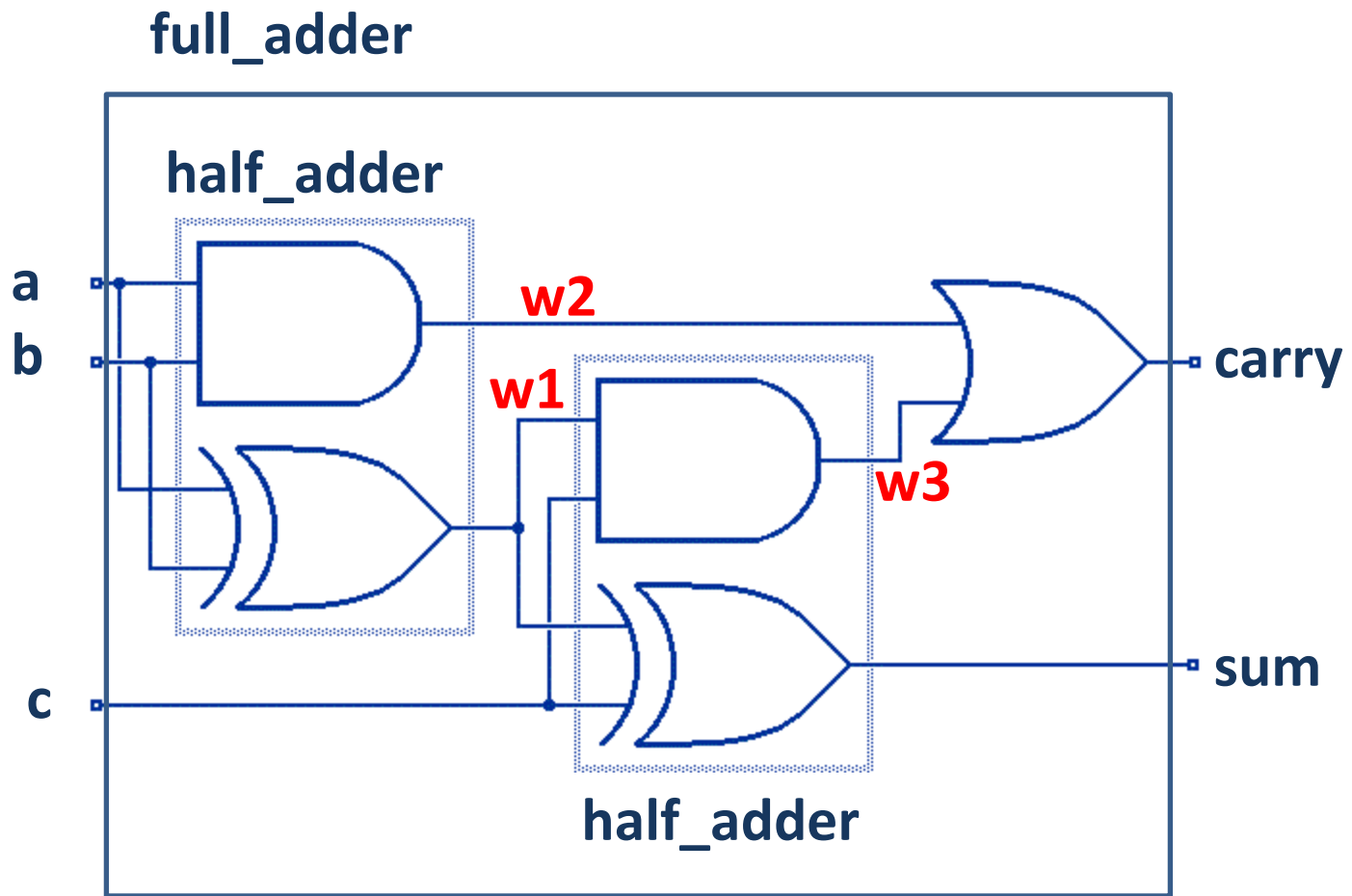



Full-Adder Circuit

```
module full_adder (sum,carry,a,b,c);
```

```
    output wire carry,sum;
```

```
    input wire a,b,c;
```

```
    wire w1,w2,w3;
```

All ports and intermediate connections become wires

```
//connect by position
```

```
//port order in ha_struct is (sum,carry,a,b)
```

```
half_adder HA0(w1,w2,a,b);
```

one to one mapping

...continued



Full-Adder Circuit

//port order in ha_struct is (sum,carry,a,b)

//connect by name

half_adder HA1(.carry(w3),

.sum(sum),

.a(w1),

.b(c));

port name

wire name


Order is unimportant

Recommended!!

or OR0(carry,w2,w3);

endmodule


Full-Adder Block Diagram

 


- Port directions are indicated visually
- Ports names are inside the box
- Entity name is outside the box

Full-Adder Hierarchical Diagram

full_adder

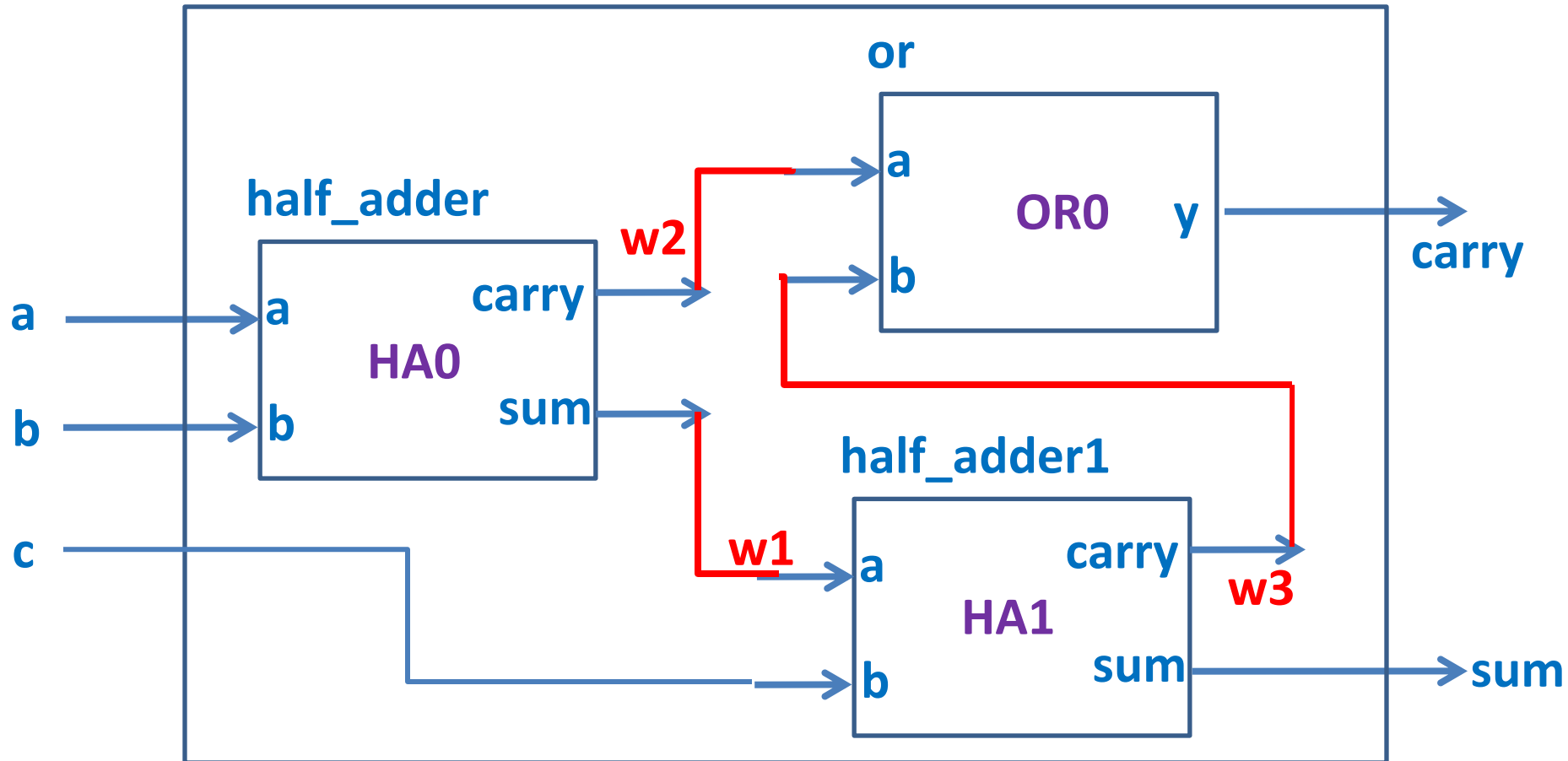


Byte Adder Block Diagram

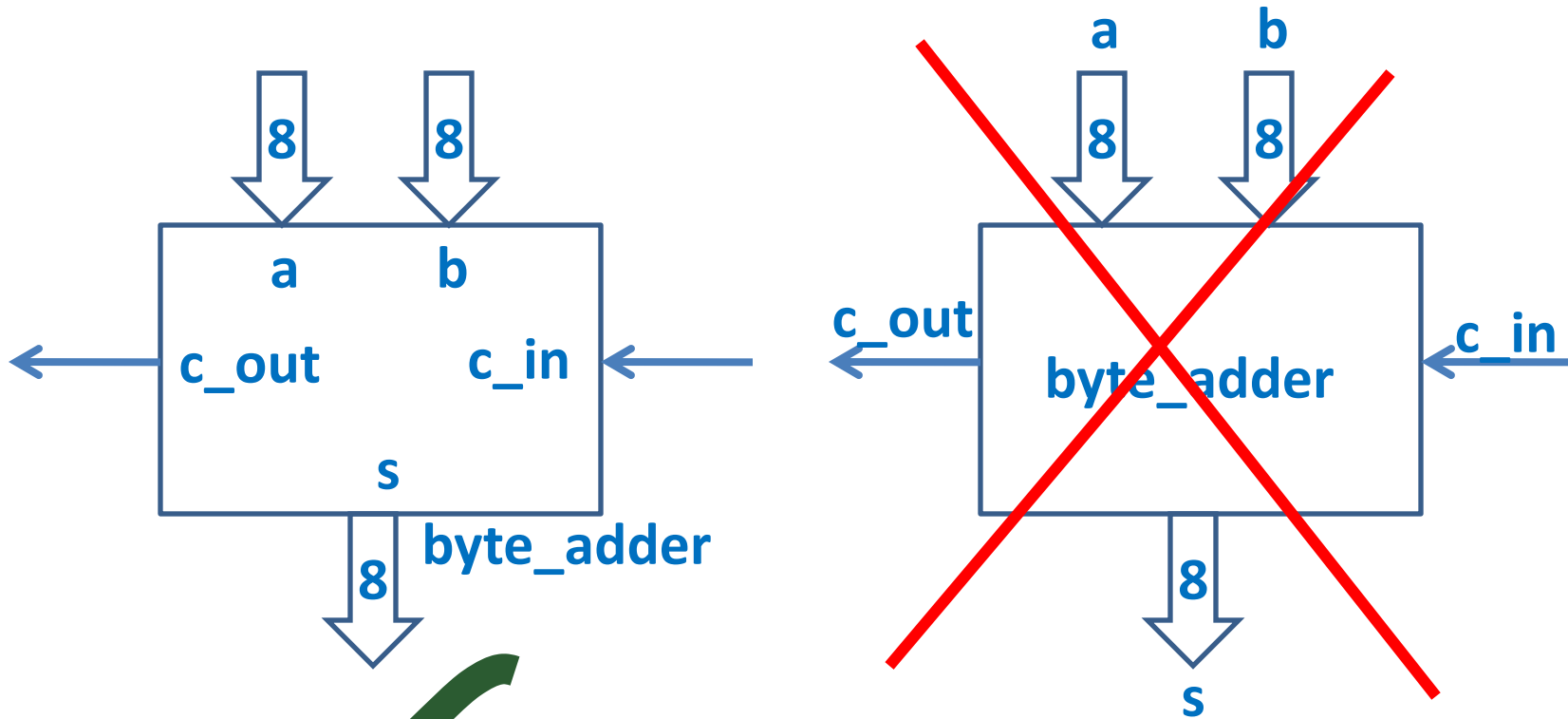

$a \rightarrow a_7a_6a_5a_4a_3a_2a_1a_0$
 $b \rightarrow b_7b_6b_5b_4b_3b_2b_1b_0$
 $s \rightarrow s_7s_6s_5s_4s_3s_2s_1s_0$



Byte Adder From Full-Adder

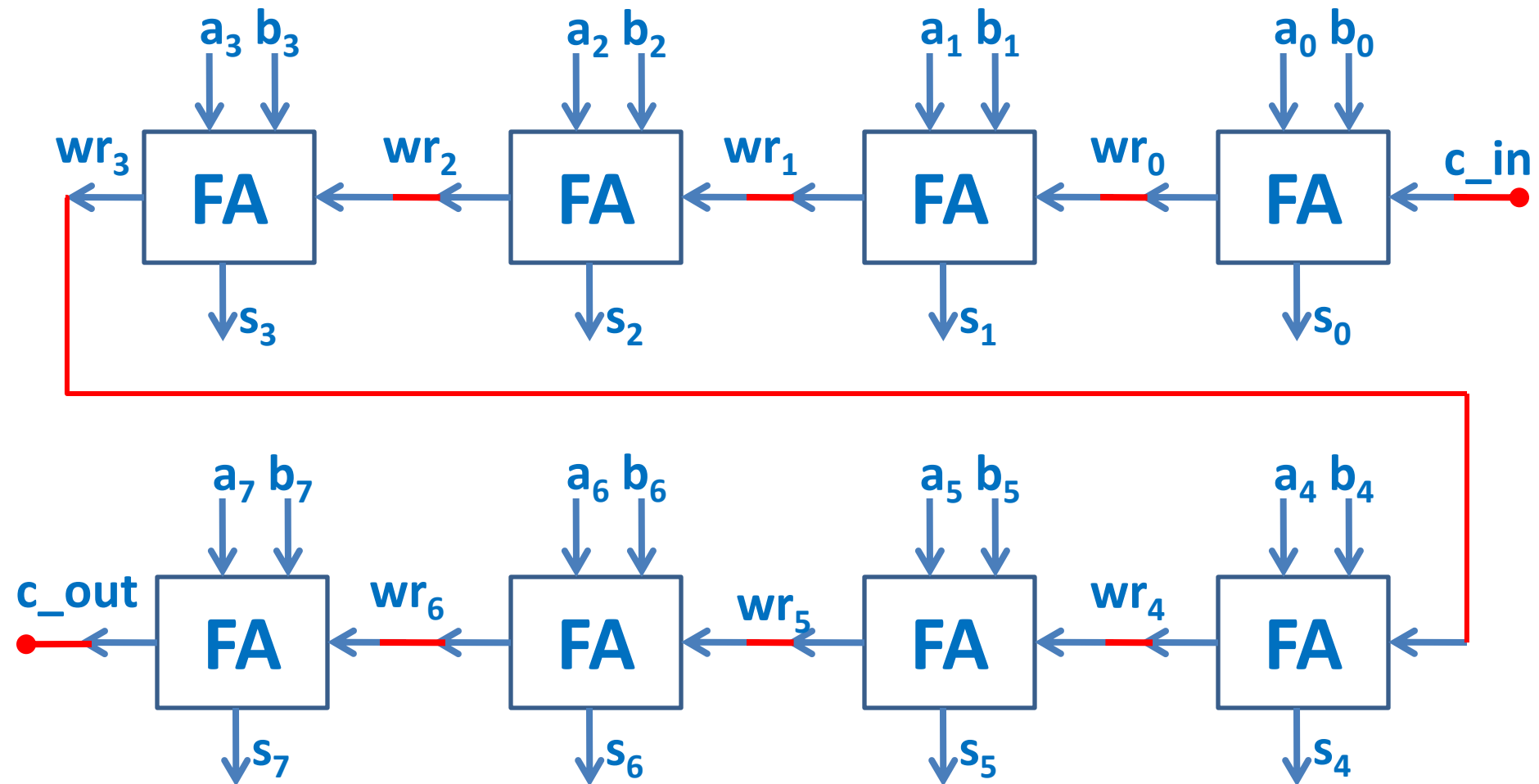



Byte-Adder in Verilog

```
module byte_adder_struct(sum, c_out, a, b, c_in);
```

```
    output wire [7:0] sum;
```

```
    output wire  c_out;
```

```
    input wire [7:0] a,b;
```

```
    input wire  c_in;
```

```
    wire [7:0] wr;
```

creates bus

```
//full adder instance for 0th bit
```

```
full_adder_beh FA_BEH_0(...);
```

```
//full adder instance for 1st bit
```

```
full_adder_beh FA_BEH_1(...);
```




Byte-Adder in Verilog

```
//full adder instance for 2nd bit
full_adder_beh FA_BEH_2(...);
//full adder instance for 3rd bit
full_adder_beh FA_BEH_3(...);
//full adder instance for 4th bit
full_adder_beh FA_BEH_4(...);
//full adder instance for 5th bit
full_adder_beh FA_BEH_5(...);
//full adder instance for 6th bit
full_adder_beh FA_BEH_6(...);
//full adder instance for 7th bit
full_adder_beh FA_BEH_7(...);
endmodule
```


Wait A Minute!!!

**Are you saying that I
will repeat code this
way even for 64-bit
adder?**

**There has to be a
better way!!!**

**Use generate for
instantiating repetitive
blocks**

A Symmetrical View of Byte-Adder

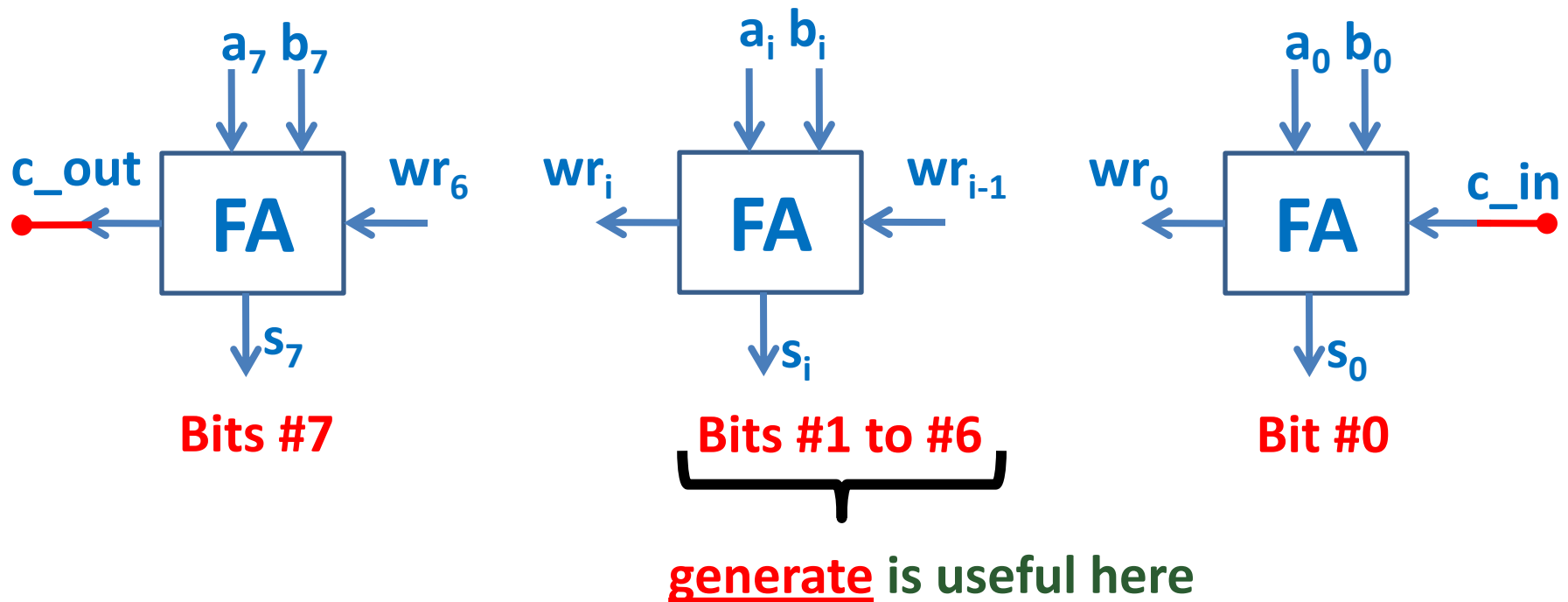



Generate Block Syntax

```
genvar i;  
generate  
    for(i = 0; i < size; i = i + 1)  
        begin  
            //generate block code  
        end  
    endgenerate
```



Byte Adder Using Generate

```
module byte_adder_struct(sum, c_out, a, b, c_in);  
    output wire [7:0] sum;  
    output wire    c_out;  
    input wire [7:0] a,b;  
    input wire    c_in;  
    wire [7:0] wr;
```

...continued



Byte Adder Using Generate

```
genvar i;
```

```
generate
```

```
  for( i = 0; i < 8; i = i + 1)
```

```
  begin
```


```
    if(i == 0)
```

```
      full_adder_beh FA_BEH (.sum(sum[i]),
```

```
        .carry(wr[i]),
```

```
        .a(a[i]),.b(b[i]),.c_in(c_in));
```

```
    ...continued
```

 


Byte Adder Using Generate

else if (i == 7)

full_adder_beh FA_BEH (.sum(sum[i]),

.carry(c_out),

.a(a[i]),.b(b[i]),.c_in(wr[i-1]));

 


else

a_i b_i full_adder_beh FA_BEH (.sum(sum[i]),

.carry(wr[i]),

.a(a[i]),.b(b[i]),.c_in(wr[i-1]));

...continued

 



Byte Adder Using Generate

```
end  
endgenerate  
endmodule
```



References

- Ciletti, Michael D., *Advanced Digital Design with Verilog HDL*, Prentice Hall India, 2003.
- Palnitkar, Samir, *Verilog HDL: A Guide to Design and Synthesis*, Sunsoft Press, 1996.
- Brad Hutchings, [Verilog – A Hardware Description Language](#), ECEn 224 Fundamentals of Digital Systems, Fall 2011, Dept. of ECE, Brigham Young University, accessed on 27.06.2012.
- Prof. Stephen A. Edwards, [Verilog 1995, 2001 and SystemVerilog 3.1](#), Languages for Embedded Systems, Spring 2009, University of Trento, Italy, accessed on 28.06.2012.
- Charles R. Kime and Michael J. Schulte, [Verilog HDL Introduction](#), ECE 554 Digital Engineering Laboratory, Fall 2009, Dept. of ECE, University of Wisconsin, Madison accessed on 27.06.2012.
- J. Wawrzynek, [CS61c: Representation of Combinational Logic Circuits](#), Lecture Notes, CS61c Great Ideas in Computer Science, Dept. of CS, University of California, Berkeley accessed on 27.06.2012.
- Full-Adder schematic diagram
<http://www.physics.udel.edu/~watson/scen103/colloq2000/fulladder.html>
accessed on 27.06.2012.



References

- Intel 4004 Microprocessor Schematic
<http://xenia.media.mit.edu/~mcnerney/2009-4004/i4004-schematic.gif>
accessed on 26.06.2012.
- ARM Mobile Computing Platform
[http://www.arm.com/images/processor/Mobile Computing Diagram 550.jpg](http://www.arm.com/images/processor/Mobile_Computing_Diagram_550.jpg) accessed on 26.06.2012.
- AMD Bull Dozer family block diagram
[http://upload.wikimedia.org/wikipedia/commons/e/ec/AMD Bulldozer block diagram %288 core CPU%29.PNG](http://upload.wikimedia.org/wikipedia/commons/e/ec/AMD_Bulldozer_block_diagram_%288_core_CPU%29.PNG) accessed on 26.06.2012
- AMD transistor count <http://news.softpedia.com/news/Ex-AMD-Engineer-Blames-Bulldozer-s-Low-Performance-on-Lack-of-Fine-Tuning-227816.shtml> accessed on 26.06.2012.
- Xilinx Vertex 6 Development Board
[http://hitechglobal.com/Boards/Virtex6 PCIExpress Board.htm](http://hitechglobal.com/Boards/Virtex6_PCIExpress_Board.htm) accessed on 26.06.2012.