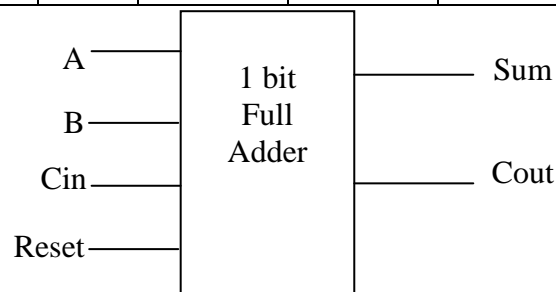


BIRLA INSTITUTE OF TECHNOLOGY & SCIENCE, PILANI K. K. BIRLA Goa Campus
Second Semester 2012-2013
IS F242 Computer Organization
Lab Handout - 1, 29th January 2013

Lab Question:

1. Given below the truth table of a 1 bit adder.

A	B	Cin	Reset	Sum	Cout
X	X	X	0	0	0
0	0	0	1	0	0
0	0	1	1	1	0
0	1	0	1	1	0
0	1	1	1	0	1
1	0	0	1	1	0
1	0	1	1	0	1
1	1	0	1	0	1
1	1	1	1	1	1



1. Implement a 1-bit full adder as given in the truth table
 - (A) Gate level model
 - (B) Data flow model and
 - (C) Behavioral model
2. Run the code in veriwell simulator with a test bench which includes all cases and checks the correctness of the design.
3. Design a 4 – bit Added / Subtractor as shown in figure below. Run the code in veriwell simulator with a test bench and check the correctness of the design.

```
module Adder1b(A, B, Cin, Reset, Sum, Cout); // 1 bit adder
```

```
module Adder4b(A4b, B4b, Cin, Reset, Sum4b, Cout); // 4 bit adder using 1 bit adder
```

```
module AddSub4b(A4b, B4b, AddSub, Reset, Sum4b, Cout); // Complement circuit,  
// 2:1 mux, and 4 bit adder
```

```
module testbench;
```

