

# **Digital Electronics and Microprocessors**

Class 15

CHHAYADEVI BHAMARE

# DIGITAL INTEGRATED CIRCUITS

```
graph TD; A[DIGITAL INTEGRATED CIRCUITS] --> B[SMALL SCALE INTEGRATION  
LESS THAN 12 GATES]; A --> C[MEDIUM SCALE INTEGRATION  
12 TO 99 GATES]; A --> D[LARGE SCALE INTEGRATION  
100 TO 9999 GATES]; B --> B1[GATES]; B --> B2[FLIP FLOPS]; C --> C1[ENCODERS  
DECODERS]; C --> C2[SHIFT  
REGISTERS]; C --> C3[MULTIPLEXERS  
DEMULTIPLEXERS]; C --> C4[ADDERS]; D --> D1[MEMORY]; D --> D2[SMALL  
MICROPROCESSORS];
```

**SMALL SCALE INTEGRATION**  
LESS THAN 12 GATES

GATES

FLIP FLOPS

**MEDIUM SCALE INTEGRATION**  
12 TO 99 GATES

ENCODERS  
DECODERS

SHIFT  
REGISTERS

MULTIPLEXERS  
DEMULTIPLEXERS

ADDERS

**LARGE SCALE INTEGRATION**  
100 TO 9999 GATES


MEMORY

SMALL  
MICROPROCESSORS

# Combinational Circuits

- Output is function of input only

i.e. no feedback

 


When **input** changes, **output** may change (after a delay)

# Combinational Circuits

 
## □ Analysis

- Given a circuit, find out its *function*
- Function may be expressed as:
  - Boolean function
  - Truth table



 
## □ Design

- Given a desired function, determine its *circuit*
- Function may be expressed as:
  - Boolean function
  - Truth table




# Analysis Procedure

## □ Boolean Expression Approach

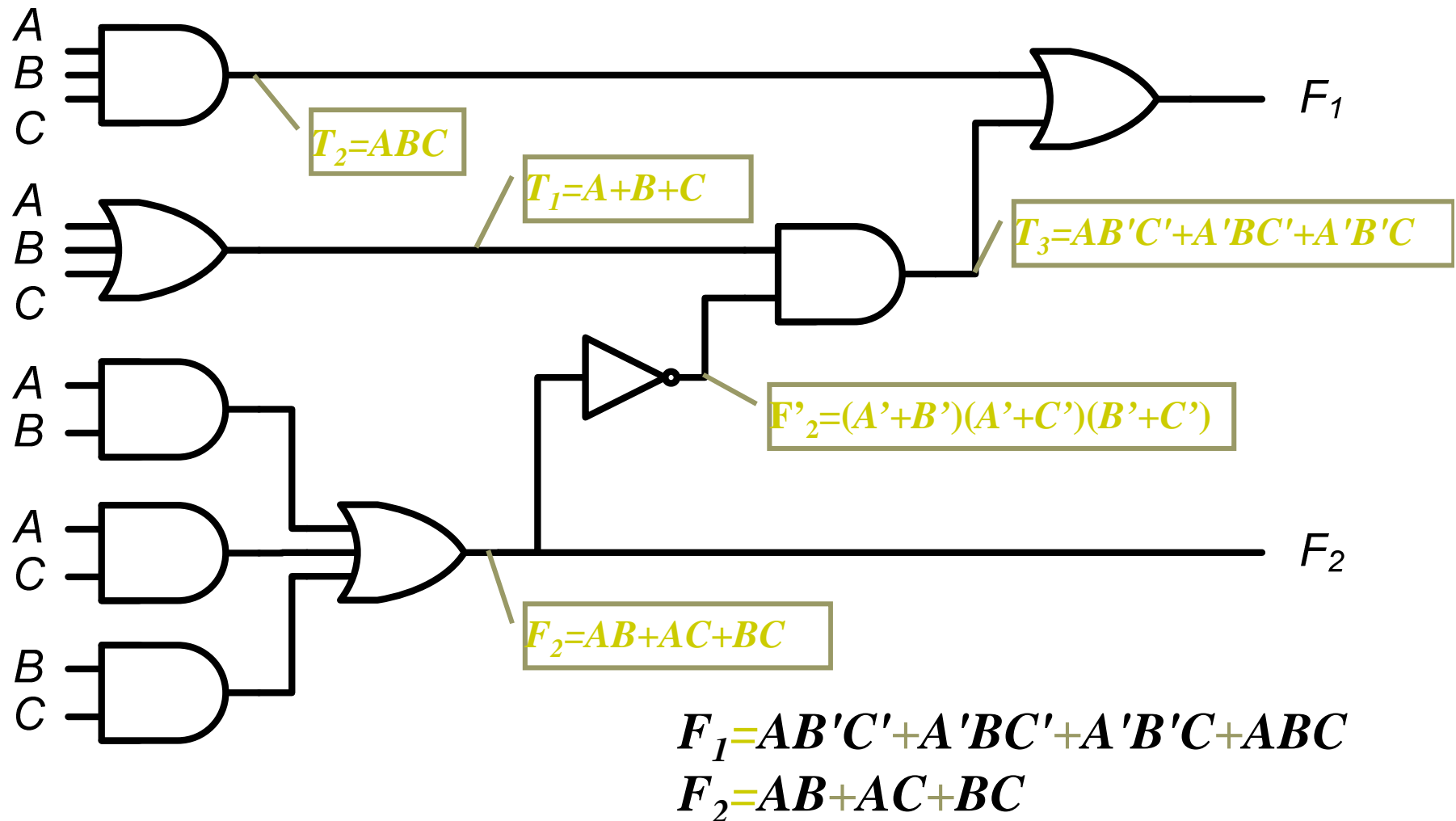


# Analysis Procedure

## □ Truth Table Approach

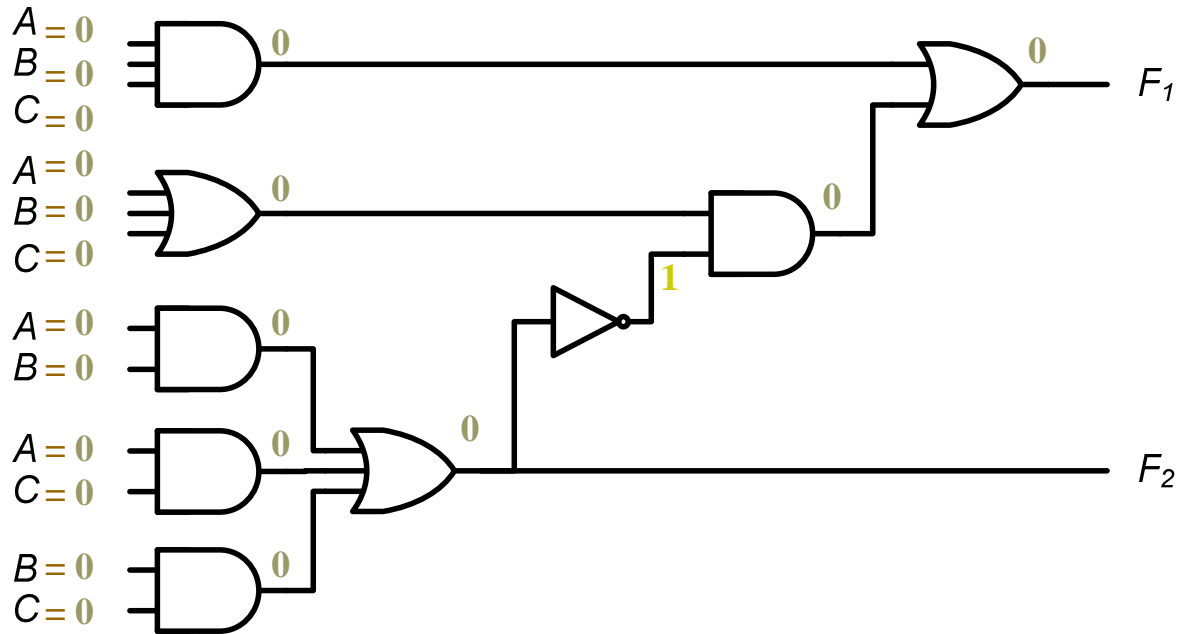[illegible]


# Analysis Procedure

## □ Truth Table Approach

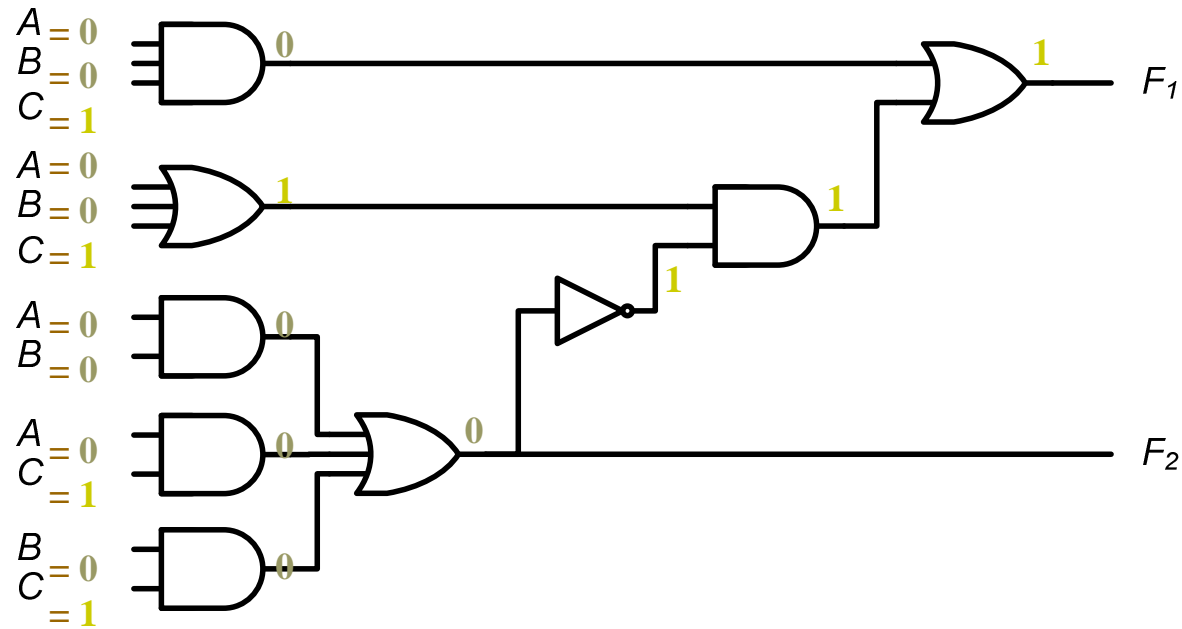[illegible]

# Analysis Procedure

## □ Truth Table Approach

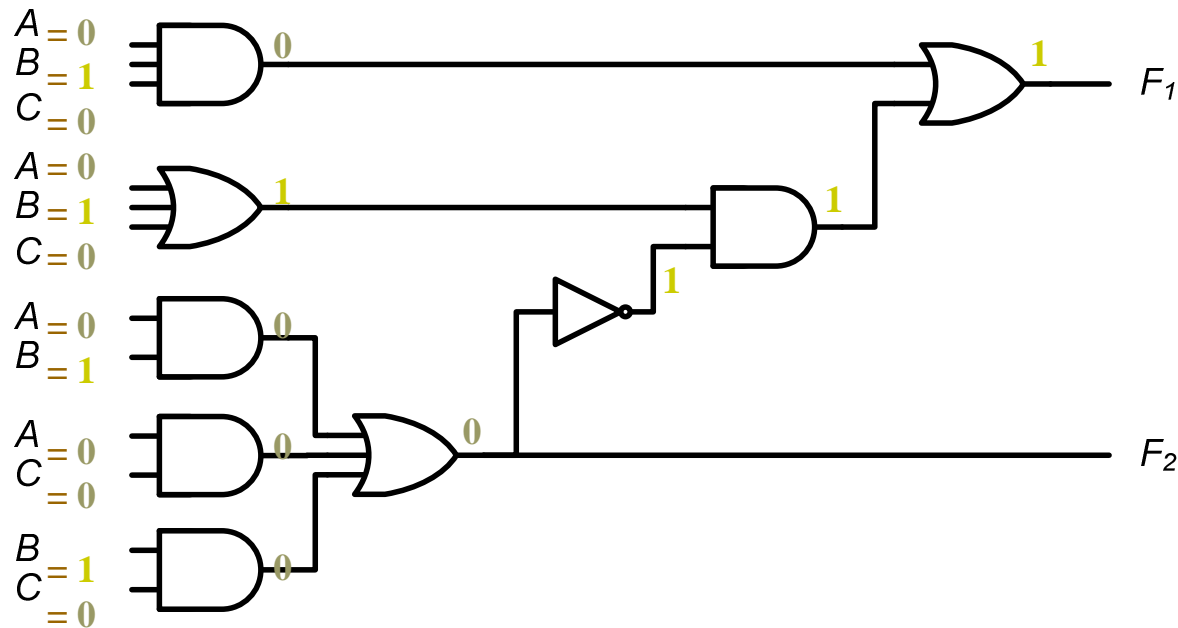


<i>A</i>	<i>B</i>	<i>C</i>	$F_1$	$F_2$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0



# Analysis Procedure


## □ Truth Table Approach

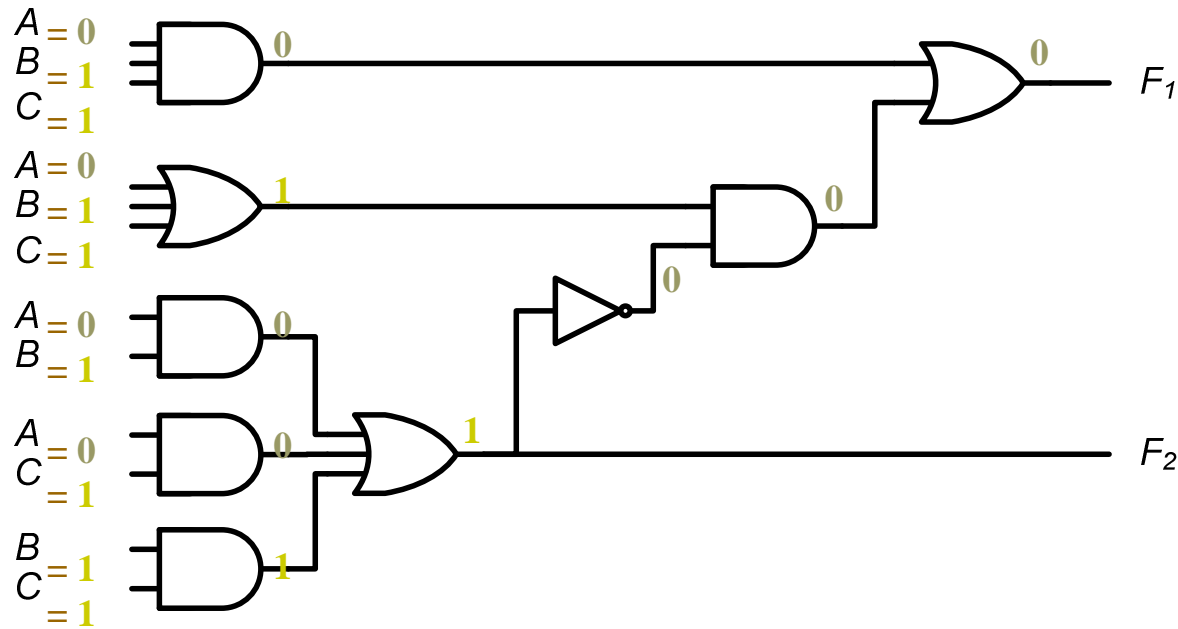

<i>A</i>	<i>B</i>	<i>C</i>	$F_1$	$F_2$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1

# Analysis Procedure


## □ Truth Table Approach

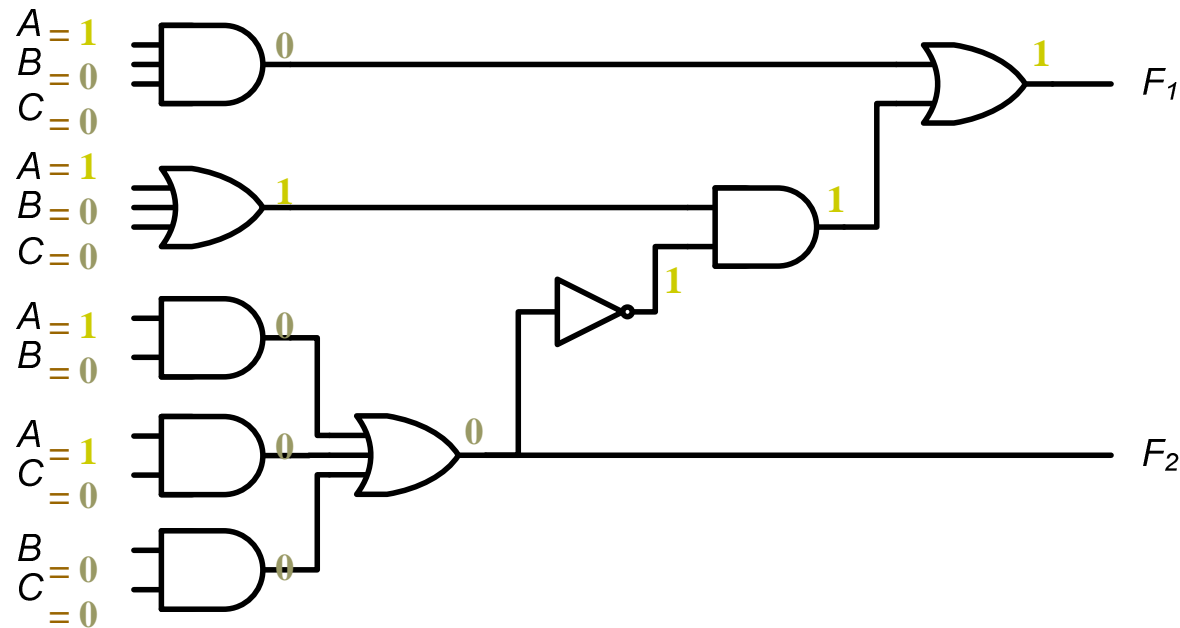

$A$	$B$	$C$	$F_1$	$F_2$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0

# Analysis Procedure


## □ Truth Table Approach

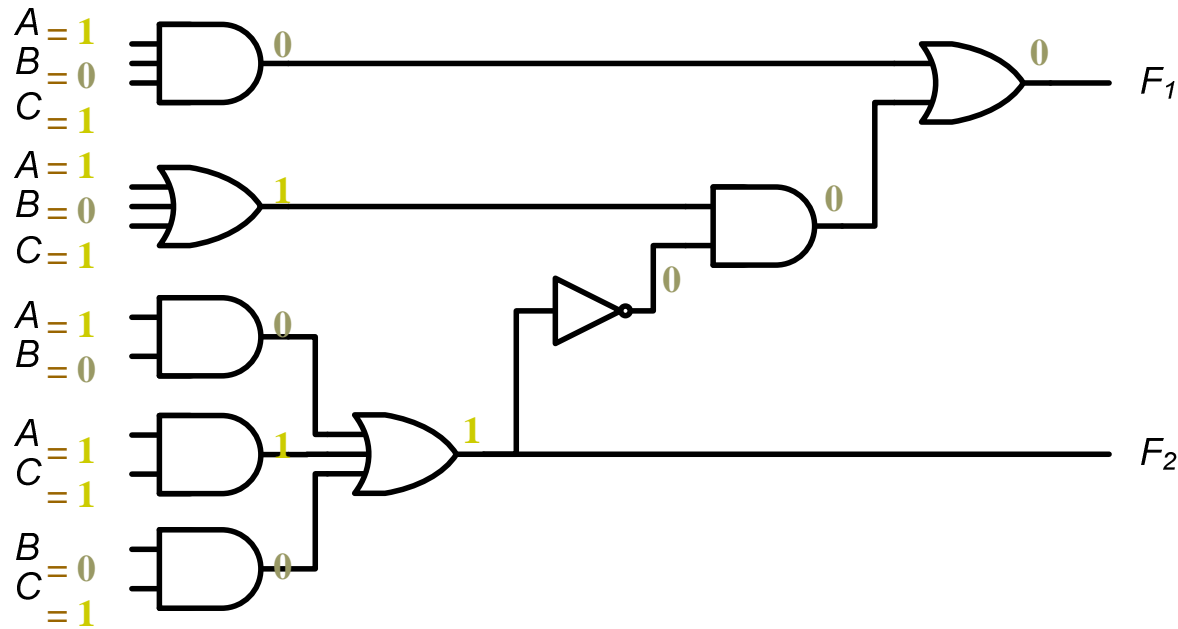

<i>A</i>	<i>B</i>	<i>C</i>	$F_1$	$F_2$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1

# Analysis Procedure


## □ Truth Table Approach

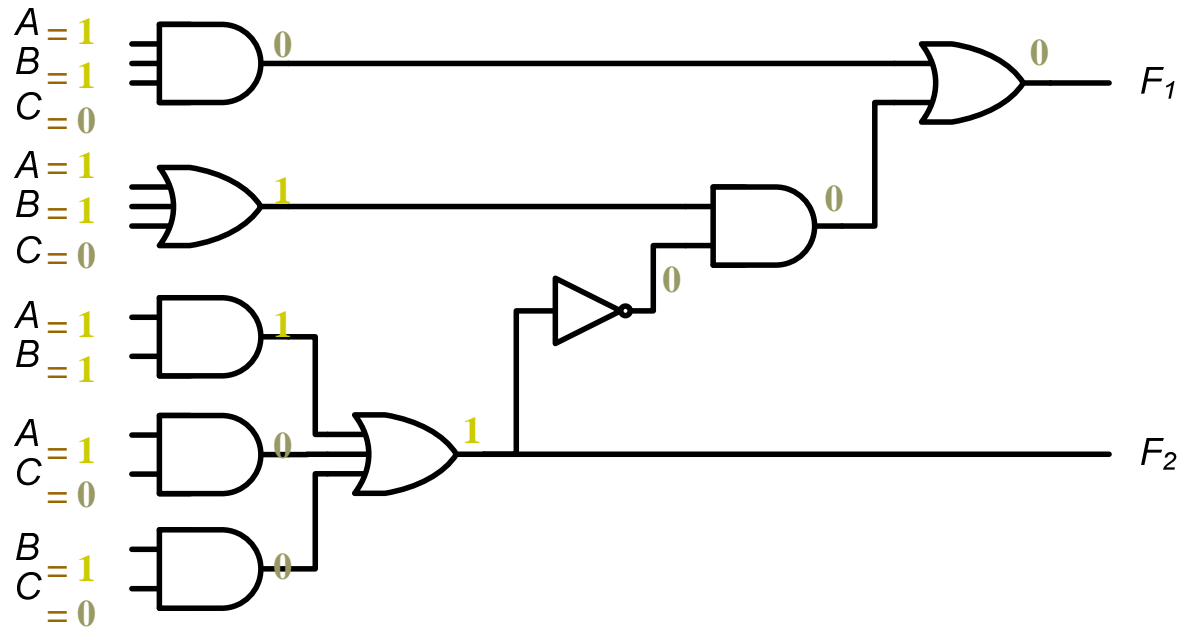

<i>A</i>	<i>B</i>	<i>C</i>	<i>F</i> <sub>1</sub>	<i>F</i> <sub>2</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1

# Analysis Procedure

## □ Truth Table Approach

 

$A$	$B$	$C$	$F_1$	$F_2$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

	$B$			
$A$	0	1	0	1
$C$	1	0	1	0

	$B$			
$A$	0	0	1	0
$C$	0	1	1	1


$$F_1 = AB'C' + A'BC' + A'B'C + ABC$$

$$F_2 = AB + AC + BC$$


# Design Procedure

## □ BCD-to-Excess 3 Converter


<i>A B C D</i>	<i>w x y z</i>
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 1 0 0
1 0 1 0	x x x x
1 0 1 1	x x x x
1 1 0 0	x x x x
1 1 0 1	x x x x
1 1 1 0	x x x x
1 1 1 1	x x x x

 


$$w = A + BC + BD$$

 

$$x = B'C + B'D + BC'D'$$

 

$$y = C'D' + CD$$

 


$$z = D'$$

# Design Procedure

## □ BCD-to-Excess 3 Converter

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	x	x	x	x
1	0	1	1	x	x	x	x
1	1	0	0	x	x	x	x
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

 

$$w = A + B(C+D)$$

$$y = (C+D)' + CD$$

$$x = B'(C+D) + B(C+D)'$$

$$z = D'$$

# MSI logic circuits(Chapter 9 of T1)

- Digital systems obtain data and information continuously operated on in some manner:
  - *Decoding/encoding.*
  - *Multiplexing/demultiplexing,.*
  - *Comparison; Code conversion;*
- These and other operations have been facilitated by the availability of numerous ICs in the MSI (medium-scale-integration) category.




# Decoders

- Decoders are used when an output or a group of outputs is to be activated only on the occurrence of a specific combination of input levels.
  - Often provided by outputs of a counter or a register.
 
# Decoders

- A **decoder** accepts a set of inputs that represents a binary number—activating only the output that corresponds to the input number.

For each of these input combinations, only one of the  $M$  outputs will be active (HIGH); all the other outputs are LOW.




Many decoders are designed to produce active-LOW outputs, where only the selected output is LOW while all others are HIGH.

# Decoders


- ❑ Extract “*Information*” from the code
- ❑ Binary Decoder
  - Example: 2-bit Binary Number

Only *one* lamp will turn on

 


# Decoders

## □ 2-to-4 Line Decoder

 

$I_1$	$I_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 

$$Y_3 = I_1 I_0$$


$$Y_2 = I_1 \bar{I}_0$$

$$Y_1 = \bar{I}_1 I_0$$

$$Y_0 = \bar{I}_1 \bar{I}_0$$

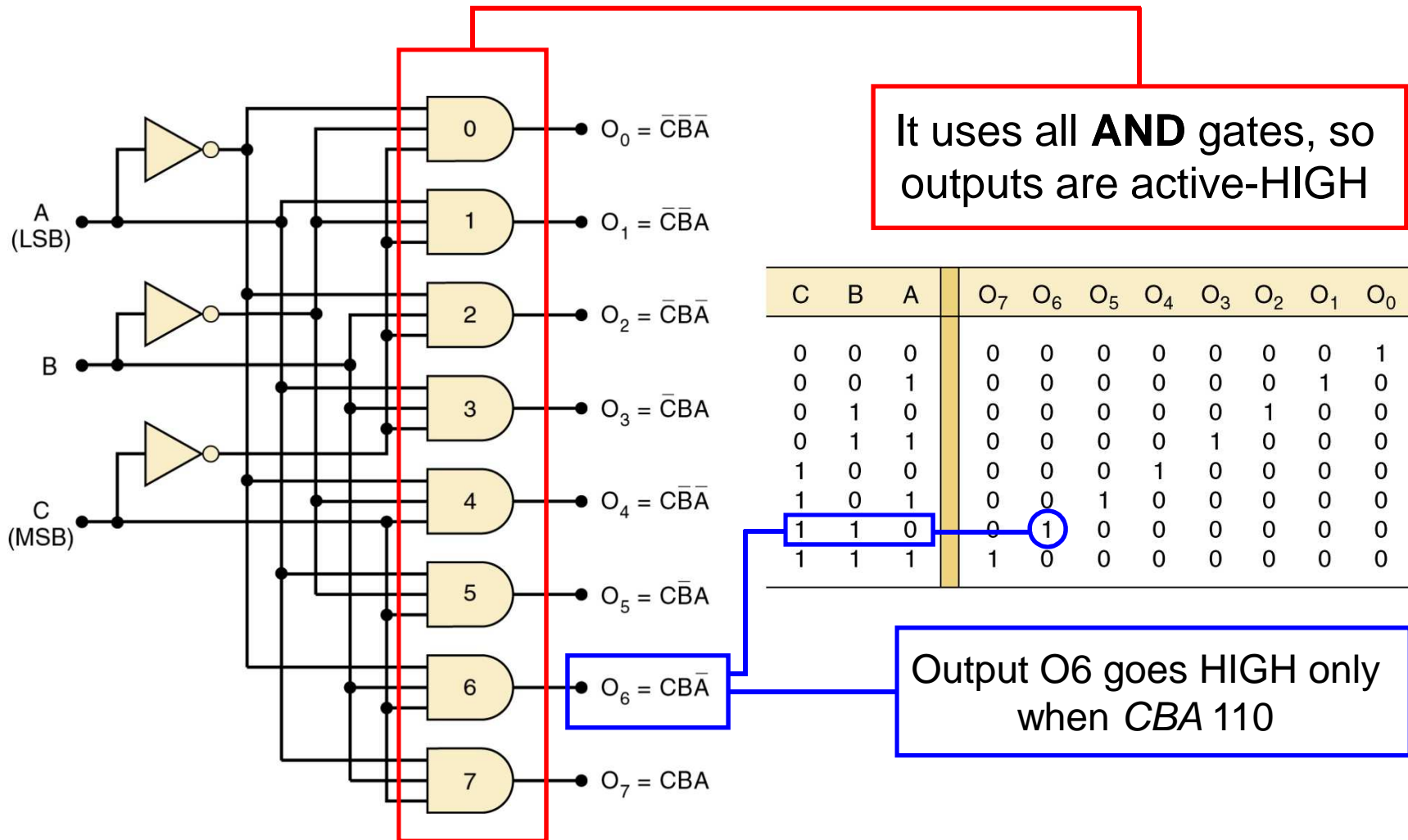
# Decoders

Circuitry for a decoder with three inputs and 8 outputs.



# Decoders

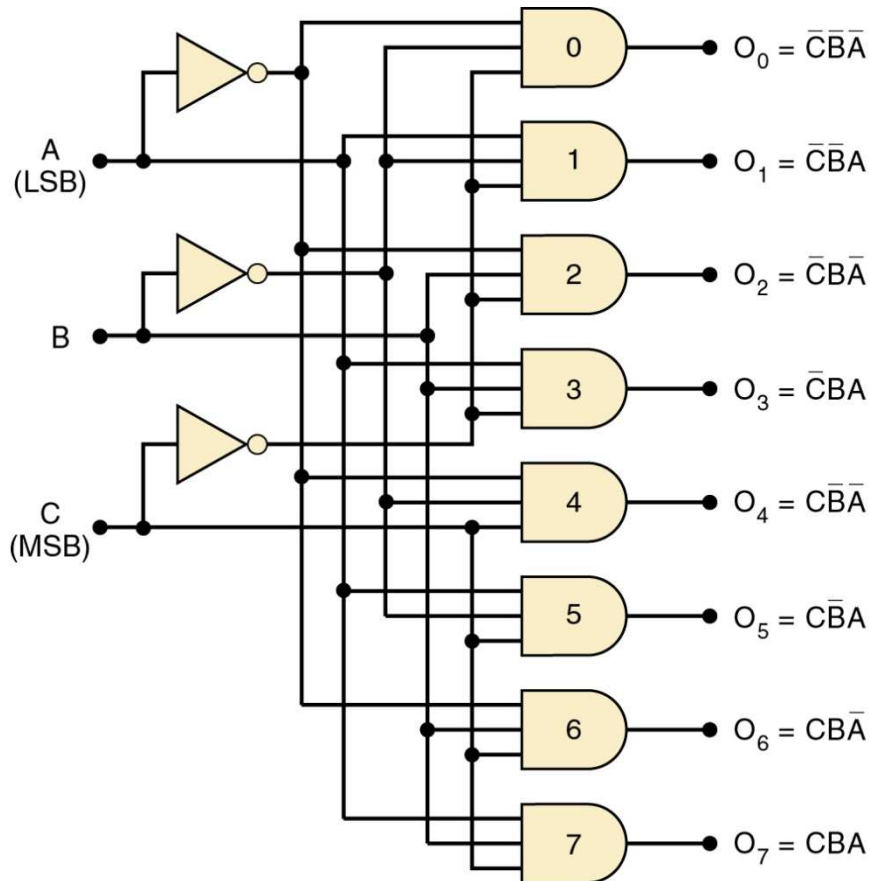**Circuitry for a decoder with three inputs and 8 outputs.**



This can be called a *3-line-to-8-line decoder*—it has three input lines and eight output lines.


Also referred to as a *1-of-8 decoder*—only 1 of the 8 outputs is activated at one time.

# Decoders


- ❑ Some decoders have one or more enable inputs used to control the operation of the decoder.
  - The decoder is enabled only if *ENABLE* is HIGH.
- ❑ With common *ENABLE* line connected to a fourth input of each gate:
  - If *ENABLE* is HIGH, the decoder functions normally.
    - ❑ *A, B, C* input will determine which output is HIGH.
  - If *ENABLE* is LOW, *all* outputs will be forced LOW.
    - ❑ *Regardless* of the levels at the *A, B, C* inputs.

# Decoders

## □ “*Enable*” Control

 

$E$	$I_1$	$I_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

 




# Decoders

## □ Expansion

$I_2 I_1 I_0$	$Y_7 Y_6 Y_5 Y_4 Y_3 Y_2 Y_1 Y_0$
0 0 0	0 0 0 0 0 0 0 1
0 0 1	0 0 0 0 0 0 1 0
0 1 0	0 0 0 0 0 1 0 0
0 1 1	0 0 0 0 1 0 0 0
1 0 0	0 0 0 1 0 0 0 0
1 0 1	0 0 1 0 0 0 0 0
1 1 0	0 1 0 0 0 0 0 0
1 1 1	1 0 0 0 0 0 0 0



 


# Decoders

□ Active-High / Active-Low

$I_1$	$I_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

$I_1$	$I_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	1	1	1	0
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	1	1	1

   


# Implementation Using Decoders

- ❑ Each output is a minterm
- ❑ All minterms are produced
- ❑ Sum the required minterms



Example: Full Adder

$$S(x, y, z) = \sum(1, 2, 4, 7)$$

$$C(x, y, z) = \sum(3, 5, 6, 7)$$

 

# Implementation Using Decoders

  

Example:-Design a magnitude comparator circuit for 2-bit binary numbers  $A=A_1A_0$  and  $B=B_1B_0$ . The outputs are  $F$ ,  $G$ , and  $H$ , where  $F$  is 1 if  $A>B$ ,  $G$  is 1 if  $A=B$ , and  $H$  is 1 if  $A<B$ .


$A_1$	$A_0$	$B_1$	$B_0$	$F(A>B)$	$G(A=B)$	$H(A<B)$
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

$$F = \Sigma(4,8,9,12,13,14)$$

$$G = \Sigma(0,5,10,15)$$



$$H = \Sigma(1,2,3,6,7,11)$$

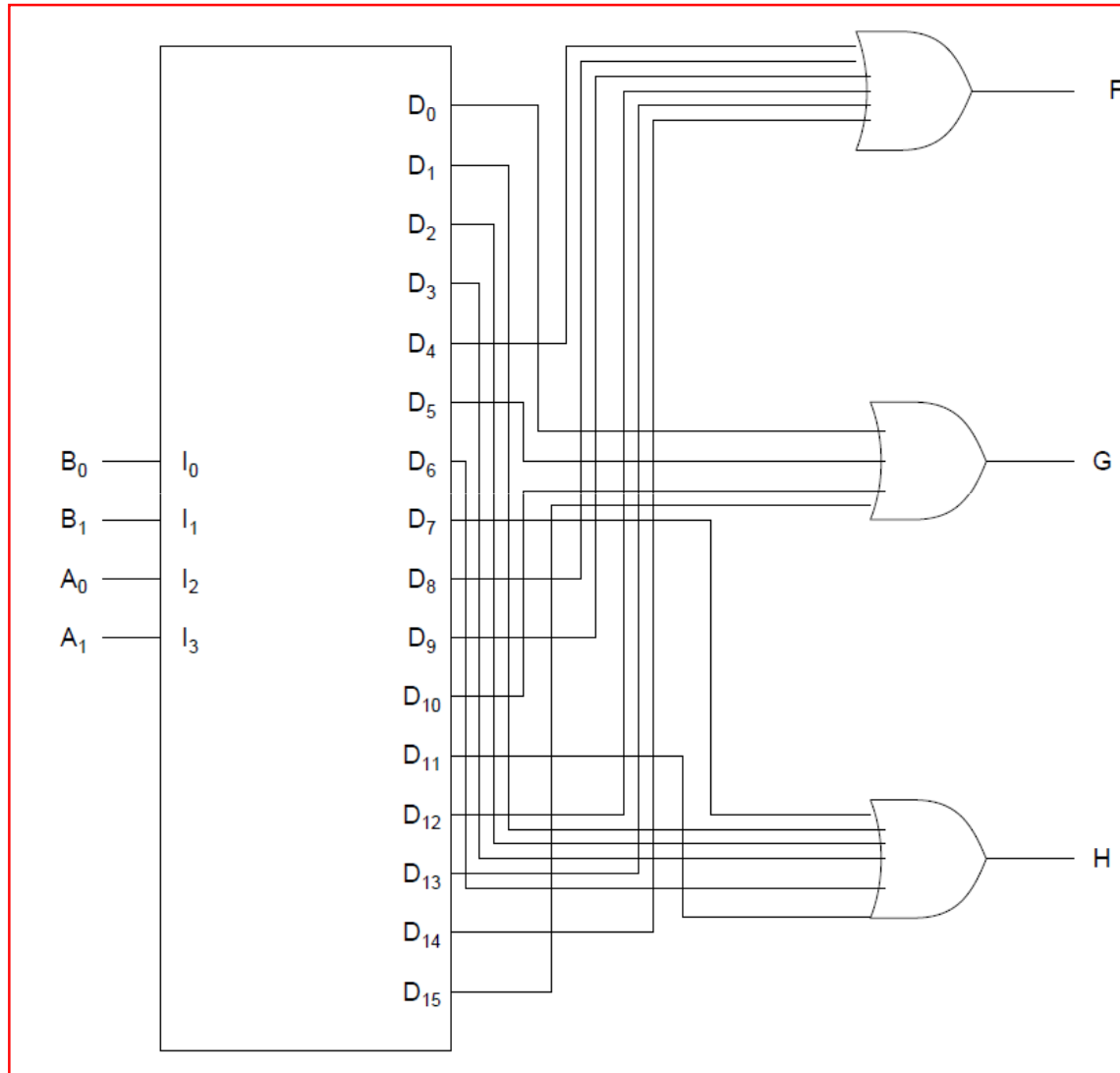Implement your comparator design using a 4-to-16 line decoder



# Seven-Segment Decoder

<i>w x y z</i>	<i>a b c d e f g</i>
0 0 0 0	1 1 1 1 1 1 0
0 0 0 1	0 1 1 0 0 0 0
0 0 1 0	1 1 0 1 1 0 1
0 0 1 1	1 1 1 1 0 0 1
0 1 0 0	0 1 1 0 0 1 1
0 1 0 1	1 0 1 1 0 1 1
0 1 1 0	1 0 1 1 1 1 1
0 1 1 1	1 1 1 0 0 0 0
1 0 0 0	1 1 1 1 1 1 1
1 0 0 1	1 1 1 1 0 1 1
1 0 1 0	x x x x x x x
1 0 1 1	x x x x x x x
1 1 0 0	x x x x x x x
1 1 0 1	x x x x x x x
1 1 1 0	x x x x x x x
1 1 1 1	x x x x x x x

  

$$a = w + y + xz + x'z'$$

$$b = \dots$$

$$c = \dots$$

$$d = \dots$$

