


Digital Electronics and Microprocessors

Class 3

CHHAYADEVI BHAMARE

Microcomputer Application:-The logic circuit in fig generates an output MEM, that is used to activate a Memory IC in a particular Microcomputer. Determine the I/P conditions necessary to activate MEM

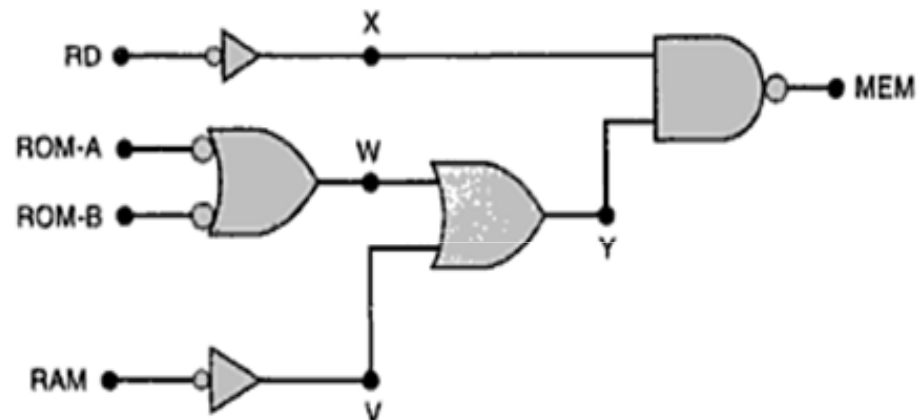1. MEM is active LOW, and it will go LOW only when x and y are HIGH
2. X will be HIGH only when RD=0.
3. Y will be high when either W or V is HIGH
4. W will be high when either ROM-A or ROM-B=0
5. V will be HIGH when RAM=0



6. Putting this all together, MEM will go LOW only when RD=0 and at least one of the three inputs ROM-A, ROM-B, or RAM is low

Implementing (synthesizing) Circuits From Boolean Expressions

- It is important to be able to draw a logic circuit from a Boolean expression.
- The expression

$$x = A \cdot B \cdot C$$

could be drawn as a three input AND gate.

- A more complex example such as

$$y = AC + B\bar{C} + \bar{A}BC$$

could be drawn as two 2-input AND gates and one 3-input AND gate feeding into a 3-input OR gate. Two of the AND gates have inverted inputs.

Reference **Example 3-7**



NOR Gates and NAND Gates

- ❑ Combine basic AND, OR, and NOT operations.
- ❑ The NOR gate is an inverted OR gate. An inversion “bubble” is placed at the output of the OR gate.
- ❑ The Boolean expression is, $x = \overline{A + B}$




NOR Gates and NAND Gates

- The NAND gate is an inverted AND gate. An inversion “bubble” is placed at the output of the AND gate.
- The Boolean expression is


$$x = \overline{AB}$$

NOR Gates and NAND Gates

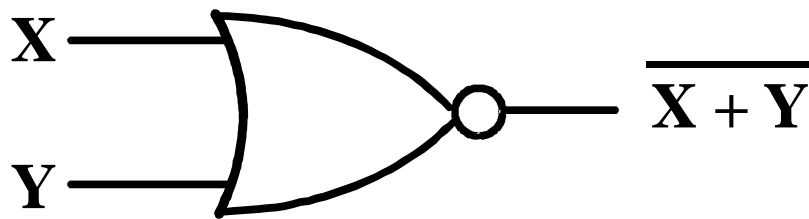- The output of NAND and NOR gates may be found by simply determining the output of an AND or OR gate and inverting it.



X	Y	NOR
0	0	1
0	1	0
1	0	0
1	1	0

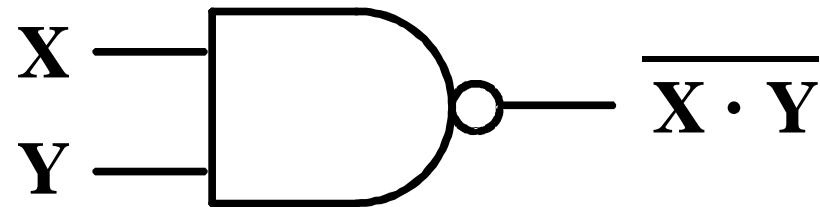

X	Y	NAND
0	0	1
0	1	1
1	0	1
1	1	0



Example:-

- Implement the logic circuit that has the expression $x = \overline{AB} \cdot (\overline{C+D})$
- Refer Examples 3-8 to 3-10 from T1



Boolean Theorems

Single Variable theorems (**Refer Fig3-25 on page 79 in T1**)

$$x \cdot 0 = 0$$

$$x \cdot 1 = x$$

$$x \cdot x = x$$

$$x \cdot \overline{x} = 0$$

$$x + 1 = 1$$

$$x + x = x$$

$$x + \overline{x} = 1$$

$$x + 0 = x$$

Boolean Theorems

- Multivariable theorems:
- Understanding all of the Boolean theorems will be useful in reducing expressions to their simplest form.

$$x + y = y + x$$

$$x \cdot y = y \cdot x$$

$$x + (y + z) = (x + y) + z = x + y + z$$

$$x(yz) = (xy)z = xyz$$

$$x(y + z) = xy + xz$$


$$(w + x)(y + z) = wy + xy + wz + xz$$

$$x + xy = x$$

$$(x + y)(x + z) = x + yz$$

$$x + \overline{x}y = x + y$$

$$\overline{x} + xy = \overline{x} + y$$



Examples:- logic simplification using Boolean theorems

- Refer Examples 3-13 to 3-15 in T1



DeMorgan's Theorems

- When the OR sum of two variables is inverted, it is equivalent to inverting each variable individually and ANDing them.



$$(x+y)' = x' \cdot y'$$

- When the AND product of two variables is inverted, it is equivalent to inverting each variable individually and ORing them.

$$(x \cdot y)' = x' + y'$$

Implications of DeMorgan's Theorems

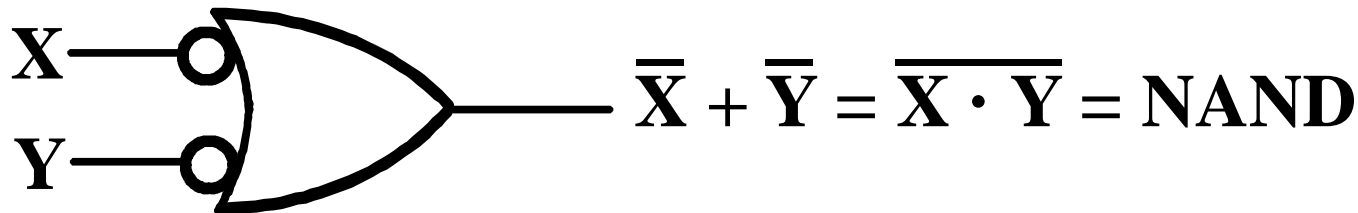
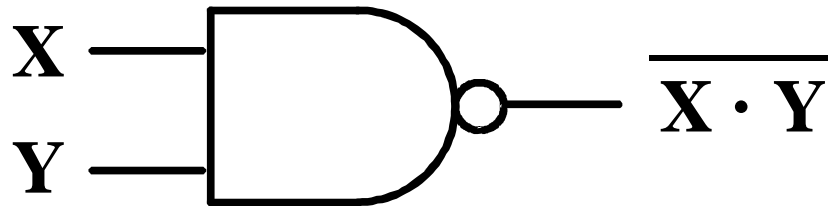
- A NAND gate is equivalent to an OR gate with inverted inputs.



Invert-OR = NAND


Implications of DeMorgan's Theorems

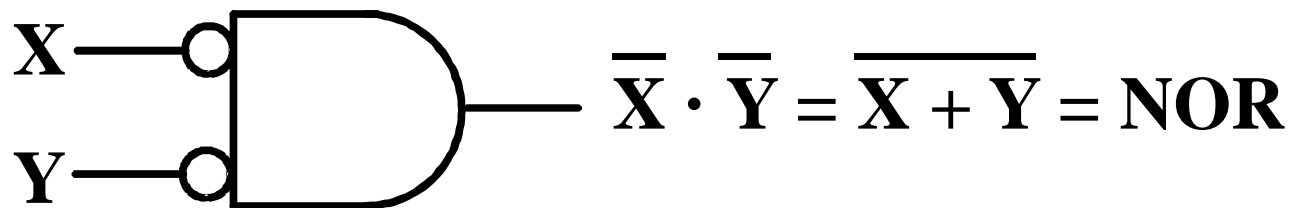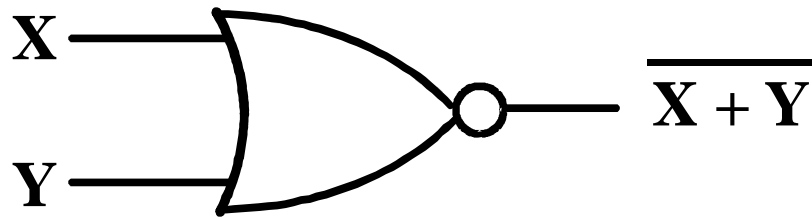- A NOR gate is equivalent to an AND gate with inverted inputs.




NOR=Invert-AND

Example

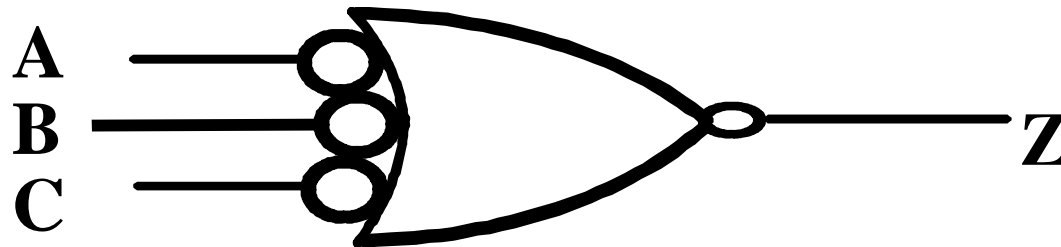

$$Z = \overline{\overline{A} + \overline{B} + \overline{C}} = ABC$$



Examples:- Simplify the following Boolean expressions using the rules of Boolean algebra

1. $W = (PQR + P'Q')(S+T) + (P' + Q')(S+T) + (S+T)$
2. $Y = (A+B)'CD + (A+B)'$
3. $H = KL' + K$



Solution:-

1. Let $x=(S+T)$, let $y=(P'+Q')$:
since $x+xy=x$, $(P'+Q')(S+T)+(S+T)=(S+T)$
 $W=(PQR+P'Q')(S+T)+(S+T) = \underline{(S+T)}$
2. work for you
3. Work for you




Universality of NAND and NOR Gates

- ❑ NAND or NOR gates can be used to create the three basic logic expressions (OR, AND, and INVERT)
- ❑ This characteristic provides flexibility and is very useful in logic circuit design.
- ❑ Examples based on this will be covered in Tut2 (refer fig 3-29 and 2-30 before coming to tut2)

IEEE/ANSI Standard Logic Symbols

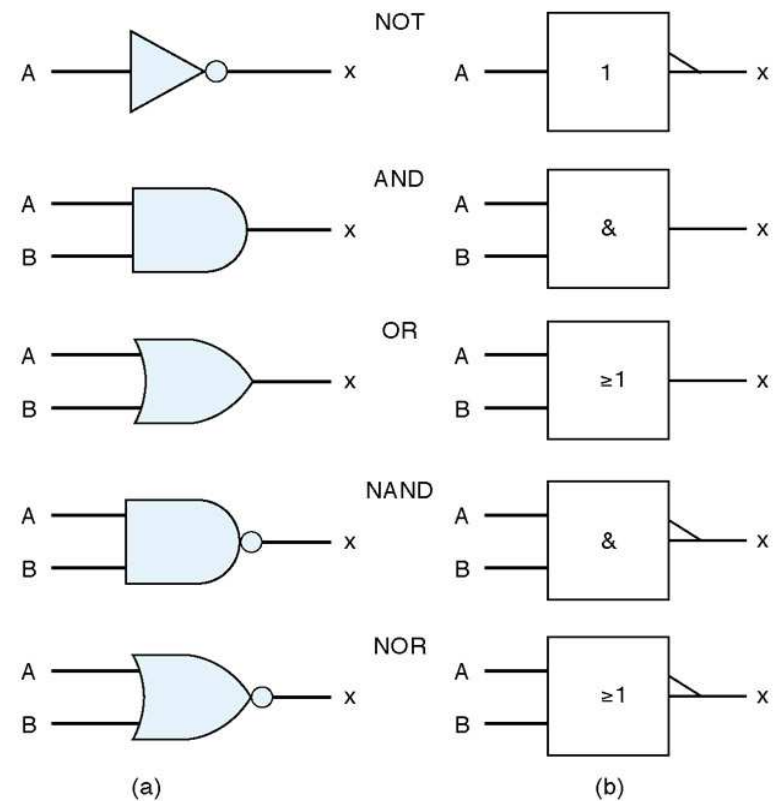- ❑ Compare the IEEE/ANSI symbols to traditional symbols.
- ❑ Rectangular symbols represent logic gates and circuits.
- ❑ A small triangle replaces the inversion bubble.
- ❑ These symbols are not widely accepted but may appear in some schematics.






Summary of Methods to Describe Logic Circuits

- The three basic logic functions are AND, OR, and NOT.
- Logic functions allow us to represent a decision process.

Examples of decision process

- If it is raining OR it looks like rain I will take an umbrella.
 - If I get paid AND I go to the bank I will have money to spend.
- Different methods to describe Logic circuits
 - Boolean Expression
 - Schematic diagram
 - Truth table
 - Timing diagram



Example:- Following English expression describing the way logic circuit needs to operate in order to drive a seatbelt warning indicator in a car

- If the driver is present **AND** the Driver in **NOT** buckled up **AND** the ignition switch is on, THEN turn on the warning light.
 - Describe the circuit using Boolean algebra, schematic diagram with logic symbols, truth table, and timing diagram

Number of Variables? 3

Driver present

Buckled up

Ignition on



Example continued (refer page 99 of T1)

1. Boolean expression

Warning light=driver present · $\overline{\text{buckled up}}$ · ignition on

2. Schematic diagram

3. Truth table



Combinational Logic (Chapter 4-T1)

- ❑ Basic logic gate functions will be combined in *combinational* logic circuits.
- ❑ Simplification of logic circuits will be done using Boolean algebra and a mapping technique.
- ❑ Troubleshooting of combinational circuits will be introduced.



Sum-of-Products Form


- A Sum-of-products (SOP) expression will appear as two or more AND terms ORed together.

$$X = ABC + \overline{A}B\overline{C}$$

$$X = AB + \overline{A}B\overline{C} + \overline{C}\overline{D} + D$$

Simplifying Logic Circuits

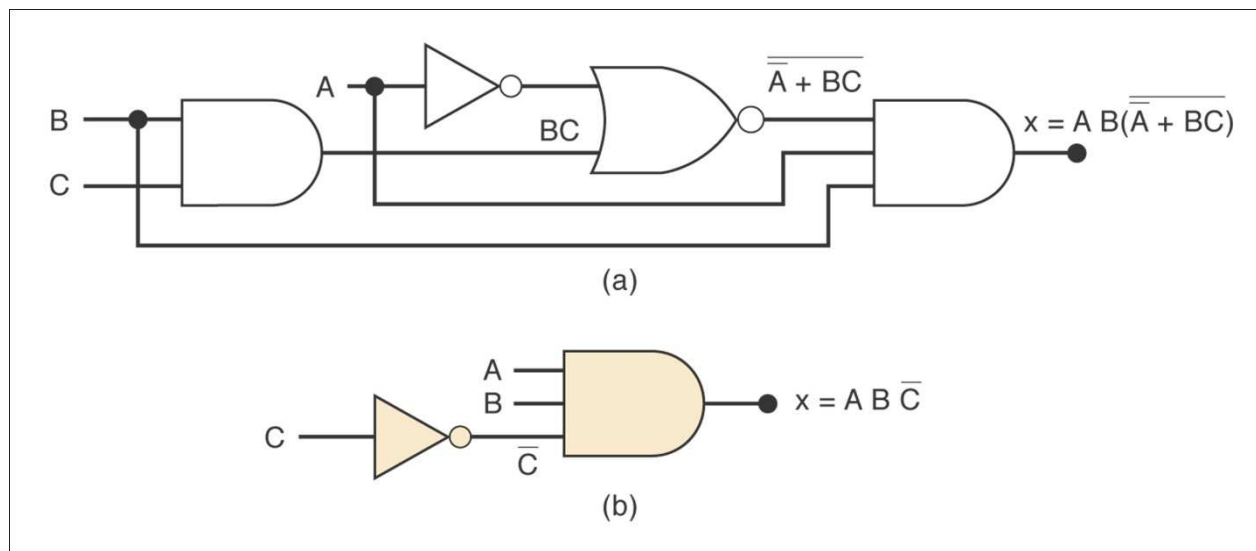- The circuits below both provide the same output, but the lower one is clearly less complex.



- We will study simplifying logic circuits using Boolean algebra and Karnaugh mapping



Algebraic Simplification

- ❑ Place the expression in SOP form by applying DeMorgan's theorems and multiplying terms.
- ❑ Check the SOP form for common factors and perform factoring where possible.
- ❑ Note that this process may involve some trial and error to obtain the simplest result.



Reference Examples for algebraic simplification

- Examples 4.1 to 4.6 from T1



Designing Combinational Logic Circuits

- To solve any logic design problem:
 - Interpret the problem and set up its truth table.
 - Write the AND (product) term for each case where the output equals 1.
 - Combine the terms in SOP form.
 - Simplify the output expression if possible.
 - Implement the circuit for the final, simplified expression.

Example application:- Majority Circuit

A logic circuit having 3 inputs, A, B, C will have its output HIGH only when a majority of the inputs are HIGH.

Step 1 Set up the truth table

A	B	C	x
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

→ $\bar{A}BC$

→ $A\bar{B}C$

→ $AB\bar{C}$

→ ABC

Step 2 Write the AND term for
each case where the output
is a 1.



Step 3 Write the SOP form the output

$$X = \overline{A}BC + A\overline{B}C + AB\overline{C} + ABC$$

Step 4 Simplify the output expression (ref. p. 119 of T1)

$$X \equiv \overline{A}BC + A\overline{B}C + AB\overline{C} + ABC$$

$$X \equiv \overline{A}BC + ABC + A\overline{B}C + ABC + AB\overline{C} + ABC$$

$$\equiv BC(\overline{A} + A) + AC(\overline{B} + B) + AB(\overline{C} + C)$$

$$\equiv BC + AC + AB$$

Step 5 Implement the circuit

