

# Digital Electronics and Microprocessors

Class 20

CHHAYADEVI BHAMARE

# Digital Arithmetic: Operations and Circuits(Chapter 6)

## Arithmetic operations

- ❑ Binary addition
- ❑ Representing Signed Numbers
- ❑ Addition and subtraction in the 2's complement systems.
- ❑ Multiplication and division of binary numbers
- ❑ BCD addition
- ❑ Hexadecimal Arithmetic

# Digital Arithmetic: Operations and Circuits(Chapter 6)

## Arithmetic Circuits

- ❑ Design of a full adder
- ❑ Parallel binary adder
- ❑ Complete parallel adder with registers
- ❑ Carry propagation
- ❑ IC arithmetic circuits (parallel adder, cascading of parallel adder, ALU IC etc)

# Signed binary numbers: Possible representations

□ Sign Magnitude:                      One's Complement                      Two's Complement

$$000 = +0$$

$$001 = +1$$

$$010 = +2$$

$$011 = +3$$

$$100 = -0$$

$$101 = -1$$

$$110 = -2$$

$$111 = -3$$

$$000 = +0$$

$$001 = +1$$

$$010 = +2$$

$$011 = +3$$

$$100 = -3$$

$$101 = -2$$

$$110 = -1$$

$$111 = -0$$

$$000 = +0$$

$$001 = +1$$

$$010 = +2$$

$$011 = +3$$

$$100 = -4$$

$$101 = -3$$


$$110 = -2$$

$$111 = -1$$


- Issues: balance, number of zeros, ease of operations
- Which one is best? Why?
- Pick the representation that made the hardware simple

# Two's complement


(let's restrict to 4 bits)

 


# Two's complement

 

# Two's complement

 


# Two's complement

 




# Two's complement

$-3 + (-6) = 7 !!$   
*Overflow*

 

# Combined Addition and Subtraction

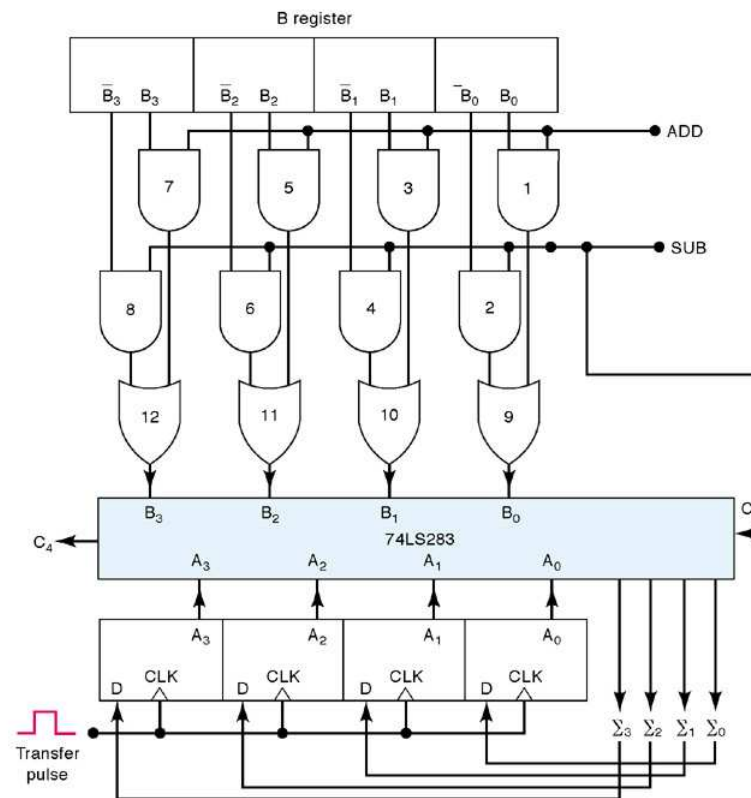

# BCD ADDER

- Add the BCD code groups for each decimal digit position; use ordinary binary addition.
- For those positions where the sum is 9 or less, the sum is in proper BCD form and no correction is needed
- When the sum of two digits is greater than 9, a correction of 0110 should be added to that sum to produce the proper BCD result. This will produce a carry to be added to the next decimal position.

■  $A_3A_2A_1A_0 \leftarrow$  BCD code group

■  $\underline{B_3}\underline{B_2}\underline{B_1}\underline{B_0} \leftarrow$  BCD code group


$S_4S_3S_2S_1S_0 \leftarrow$  straight binary sum

# Truth table

$S_4$	$S_3$	$S_2$	$S_1$	$S_0$	
0	1	0	1	0	(10)
0	1	0	1	1	(11)
0	1	1	0	0	(12)
0	1	1	0	1	(13)
0	1	1	1	0	(14)
0	1	1	1	1	(15)
1	0	0	0	0	(16)
1	0	0	0	1	(17)
1	0	0	1	0	(18)

$$X = S_4 + S_3(S_2 + S_1)$$

# A BCD adder

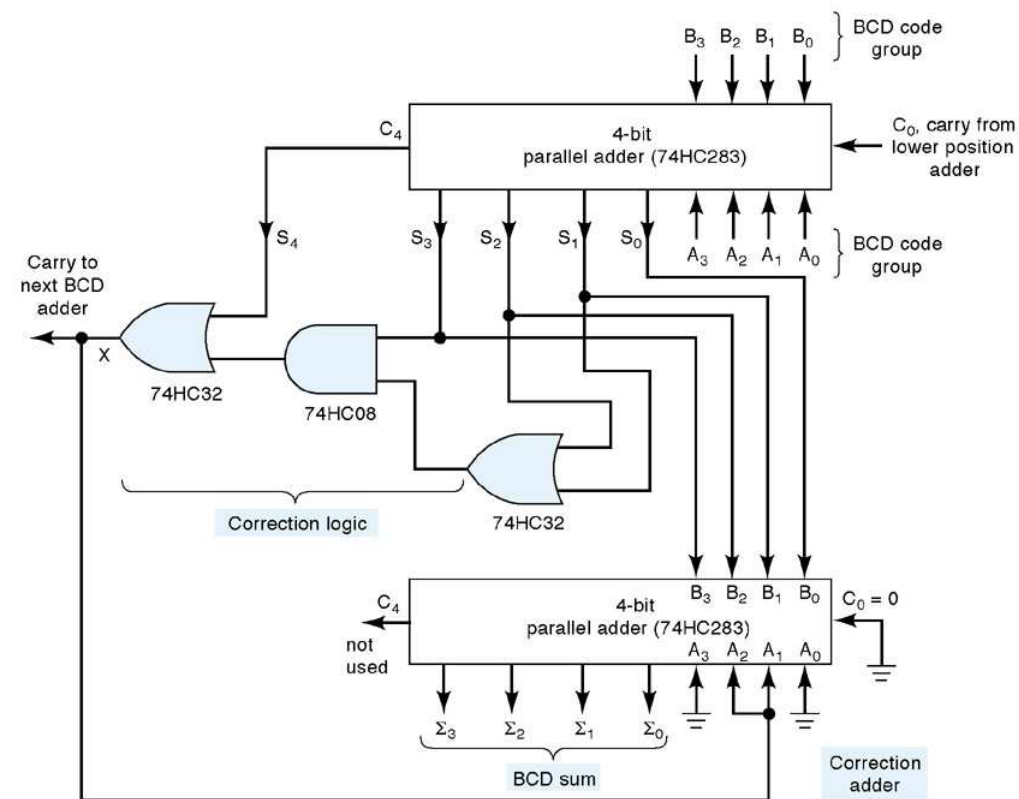


 



Fig. 4-14 Block Diagram of a BCD Adder
 
# Example

- Determine the inputs and outputs when the below circuit is used to add  $538_{10}$  to  $247_{10}$ . Assume CARRY IN=0.




# ALU(1 bit)

 



# ALU(4-Bit) Integrated Circuits

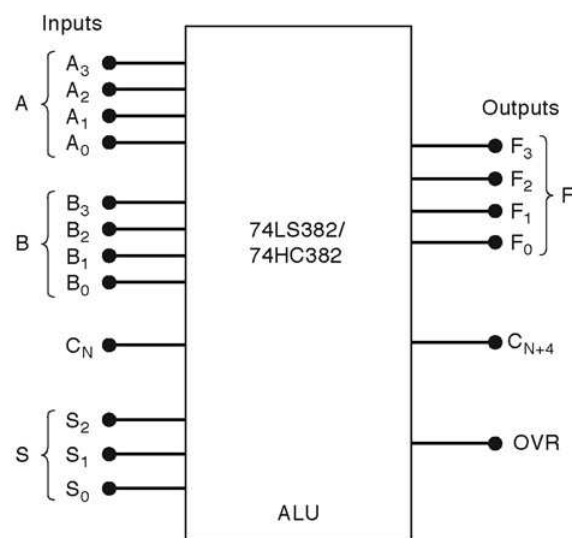

A = 4-bit input number  
 B = 4-bit input number  
 C<sub>N</sub> = carry into LSB position  
 S = 3-bit operation select inputs

F = 4-bit output number  
 C<sub>N+4</sub> = carry out of MSB position  
 OVR = overflow indicator

(a)

Function Table

S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	Operation	Comments
0	0	0	CLEAR	F <sub>3</sub> F <sub>2</sub> F <sub>1</sub> F <sub>0</sub> = 0000
0	0	1	B minus A	} Needs C <sub>N</sub> = 1
0	1	0	A minus B	
0	1	1	A plus B	Needs C <sub>N</sub> = 0
1	0	0	A ⊕ B	Exclusive-OR
1	0	1	A + B	OR
1	1	0	AB	AND
1	1	1	PRESET	F <sub>3</sub> F <sub>2</sub> F <sub>1</sub> F <sub>0</sub> = 1111


Notes: S inputs select operation.  
 OVR = 1 for signed-number overflow.

(b)

# Operations

- CLEAR
- ADD
- SUBTRACT
- XOR
- OR
- AND
- PRESET

# Expanding the ALU

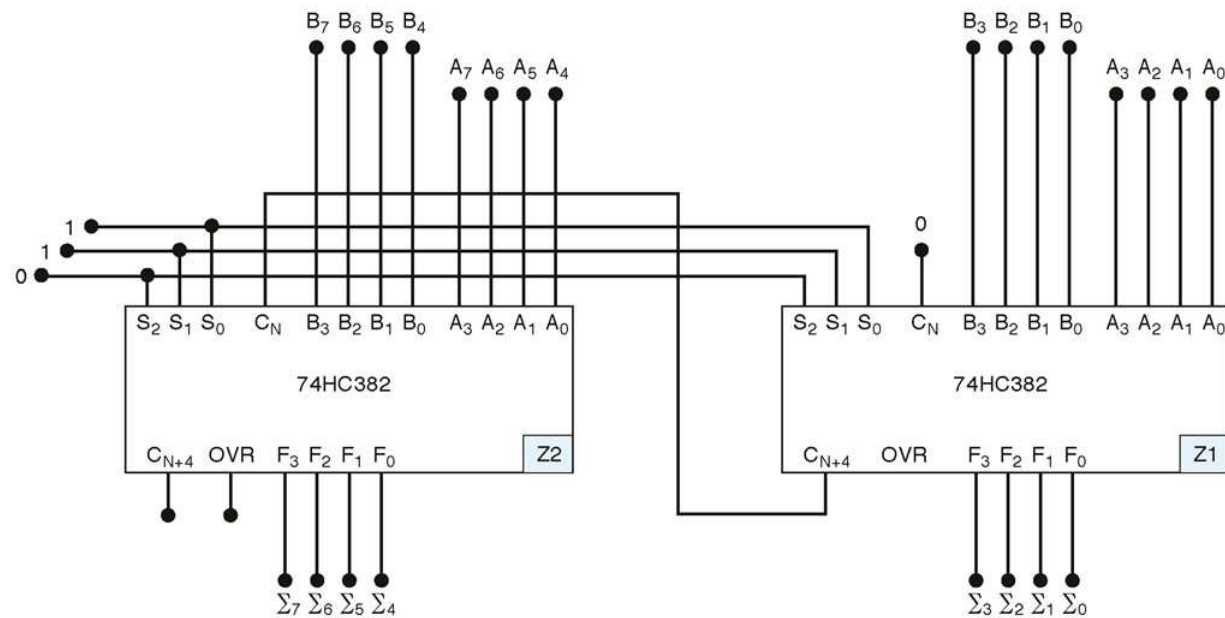

Notes: Z1 adds lower-order bits.  
 Z2 adds higher-order bits.  
 $\Sigma_7$ – $\Sigma_0$  = 8-bit sum.  
 OVR of Z2 is 8-bit overflow indicator.

# Assignment 3



6-26 to 6-39