


Digital Electronics and Microprocessors

Class 10

CHHAYADEVI BHAMARE


Flip-Flop Applications

 - Examples of applications:
 - Counting
 - Storing binary data
 - Transferring binary data between locations
- Many FF applications are categorized as sequential, which means that the output follows a predetermined sequence of states.



D	$Q(t+1)$
0	0
1	1

$$Q(t+1) = D$$

 

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$Q'(t)$

$$Q(t+1) = JQ' + K'Q$$

Frequency Division and Counting

- FFs are often used to divide a frequency. Here the output frequency is $1/8^{\text{th}}$ the input (clock) frequency.
- The same circuit is also acting as a binary counter. The outputs will count from 000_2 to 111_2 or 0_{10} to 7_{10}
- The number of states possible in a counter is the modulus or MOD number. The figure is a MOD-8 (2^3) counter. If another FF is added it would become a MOD-16 (2^4) counter.

J-K flip-flops wired as a three-bit binary counter (MOD-8).


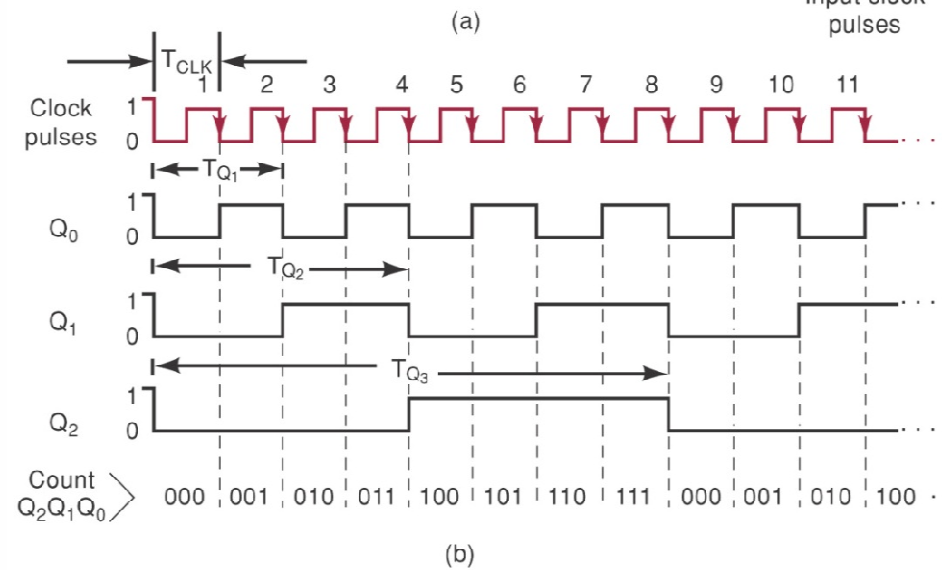
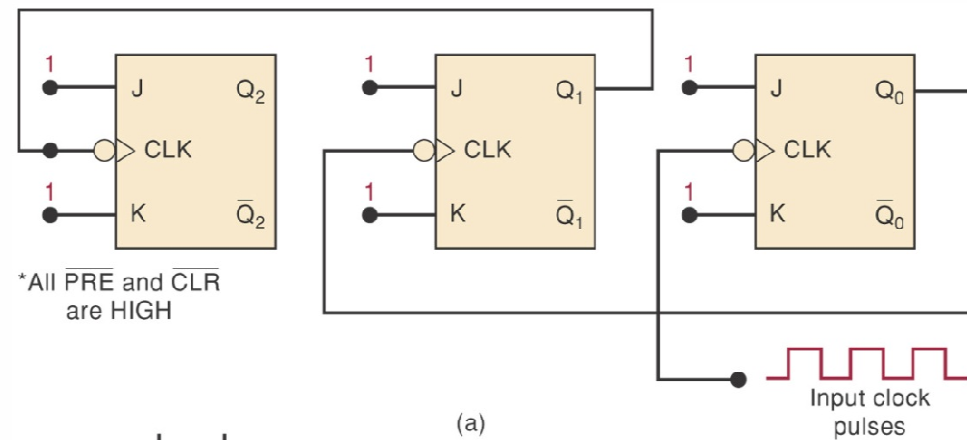


Table of flip-flop states shows binary counting sequence.

2^2	2^1	2^0	
Q_2	Q_1	Q_0	
0	0	0	Before applying clock pulses
0	0	1	After pulse #1
0	1	0	After pulse #2
0	1	1	After pulse #3
1	0	0	After pulse #4
1	0	1	After pulse #5
1	1	0	After pulse #6
1	1	1	After pulse #7
0	0	0	After pulse #8 recycles to 000
0	0	1	After pulse #9
0	1	0	After pulse #10
0	1	1	After pulse #11
.	.	.	.
.	.	.	.
.	.	.	.

 State transition diagram shows how the states of the counter flip-flops change with each applied clock pulse.



* **Note:** each arrow represents the occurrence of a clock pulse


Data Storage and Transfer

- ❑ FFs are commonly used for storage and transfer of data in binary form.
- ❑ Groups of FFs used for storage are registers.
- ❑ Data transfers take place when data is moved between registers or FFs.
- ❑ Synchronous transfers take place at PGT or NGT of clock.

Data Storage and Transfer

- ❑ Asynchronous transfers are controlled by PRE and CLR inputs.
- ❑ Transferring the bits of a register simultaneously is a parallel transfer.
- ❑ Transferring the bits of a register a bit at a time is a serial transfer.


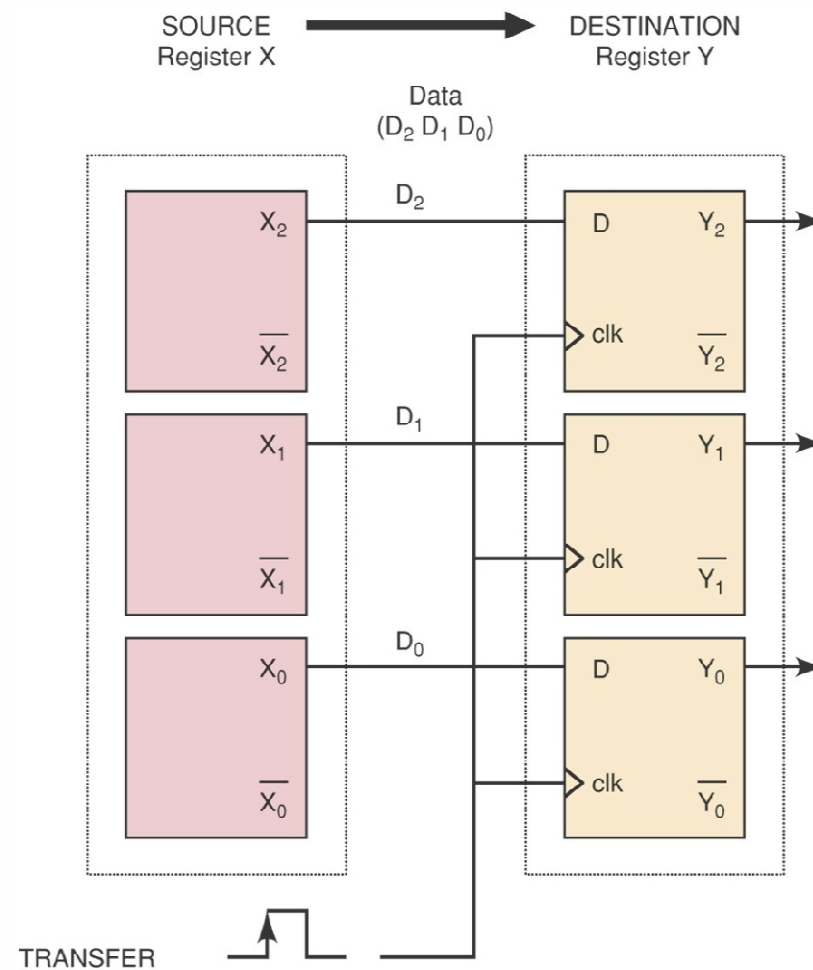
Parallel transfer of contents of register X into register Y .




Serial Data Transfer: Shift Registers

- When FFs are arranged as a shift register, bits will shift with each clock pulse.
- The direction of data shifts will depend on the circuit requirements and the design.

Four-bit shift register.

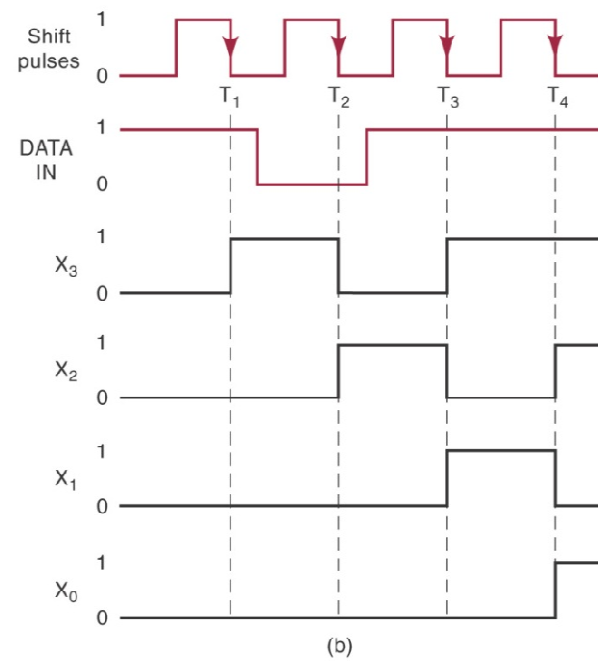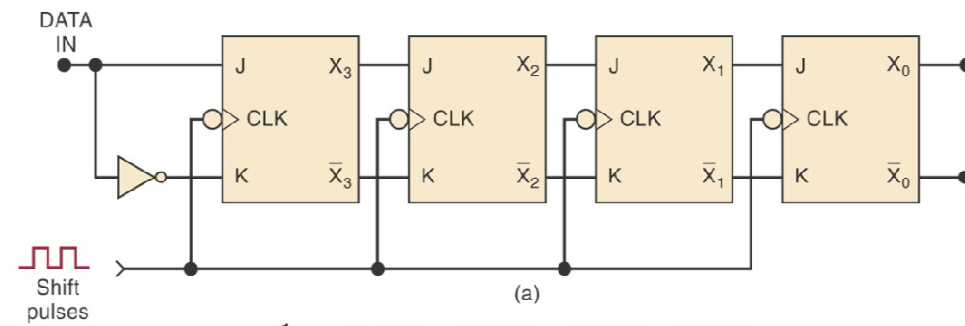

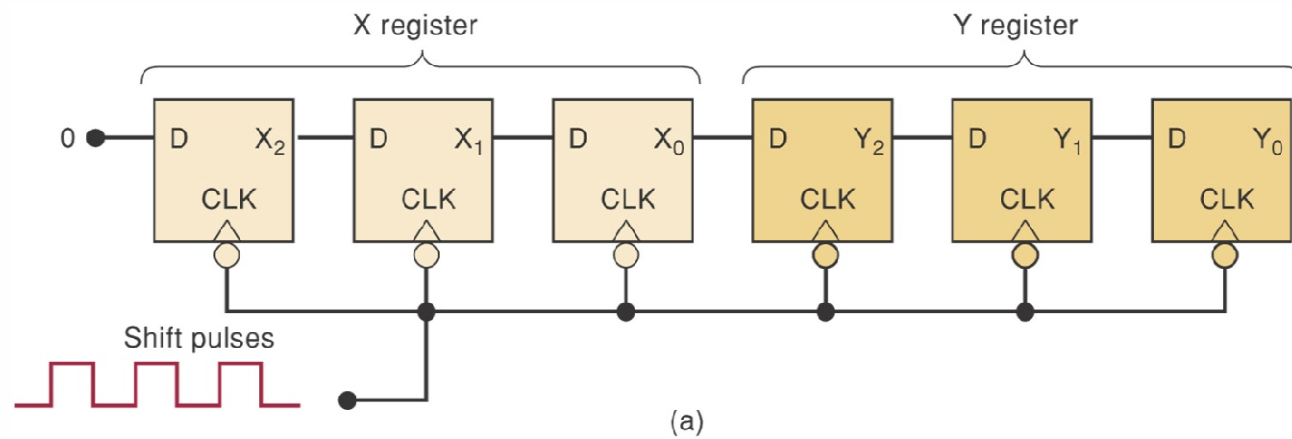Serial transfer of information from X register into Y register.



X_2	X_1	X_0	Y_2	Y_1	Y_0	
1	0	1	0	0	0	Before pulses applied
0	1	0	1	0	0	After first pulse
0	0	1	0	1	0	After second pulse
0	0	0	1	0	1	After third pulse

(b)

Serial Data Transfer: Shift Registers

- ❑ Parallel transfers – register contents are transferred simultaneously with a single clock cycle.
- ❑ Serial transfers – register contents are transferred one bit at a time, with a clock pulse for each bit.
- ❑ Serial transfers are slower, but the circuitry is simpler. Parallel transfers are faster, but circuitry is more complex.
- ❑ Serial and parallel are often combined to exploit the benefits of each.

More on Counter

Categories of counters

1. Ripple counters

The flip-flop output transition serves as a source for triggering other flip-flops

⇒ no common clock pulse (not synchronous)

2. Synchronous counters:

The CLK inputs of all flip-flops receive a common clock


Synchronous/Asynchronous Counter

Synchronous counter:

All flip-flops in a synchronous counter receive the same clock pulse and so change state simultaneously.

Asynchronous (Ripple) counter:

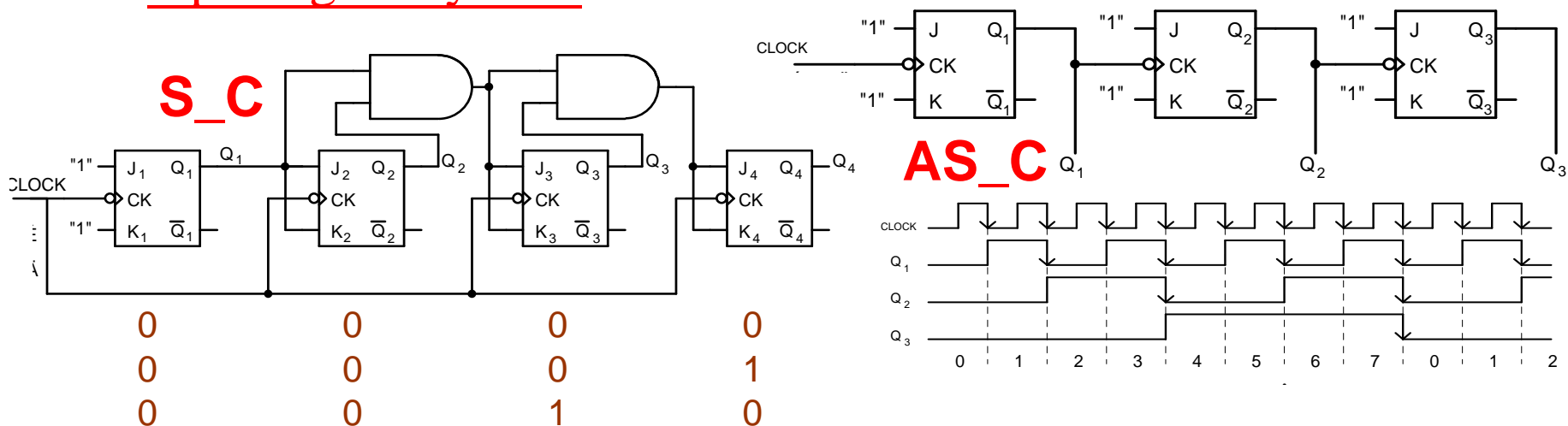Flip-flops transitions ripple through from one flip-flop to the next in sequence until all flip-flops reach a new stable value (state). Each single flip-flop stage divides the frequency of its input signal by two.



What good are counters?

- Counters can act as simple clocks to keep track of “time.”
- You may need to record how many times something has happened.
 - How many bits have been sent or received?
 - How many steps have been performed in some computation?
- All processors contain a **program counter**, or **PC**.
 - Programs consist of a list of instructions that are to be executed one after another (for the most part).
 - The PC keeps track of the instruction currently being executed.
 - The PC increments once on each clock cycle, and the next program instruction is then executed.

Some important terms

- ❑ Modulus of a counter:-the number of states through which a counter sequences before repeating.
- ❑ Full sequence counter.
- ❑ Truncated sequence counter.

Counters


- ❑ Analysis of counter:-counter circuit is given analyzing its count sequence.
- ❑ Design of a counter:-counter behavior will be given, then designing a circuit accordingly to get expected counter behavior.

Analysis of a counter

4-bit Binary Counter

A3	A2	A1	A0
0	0	1	1
0	1	0	0

Four-bit synchronous binary counter

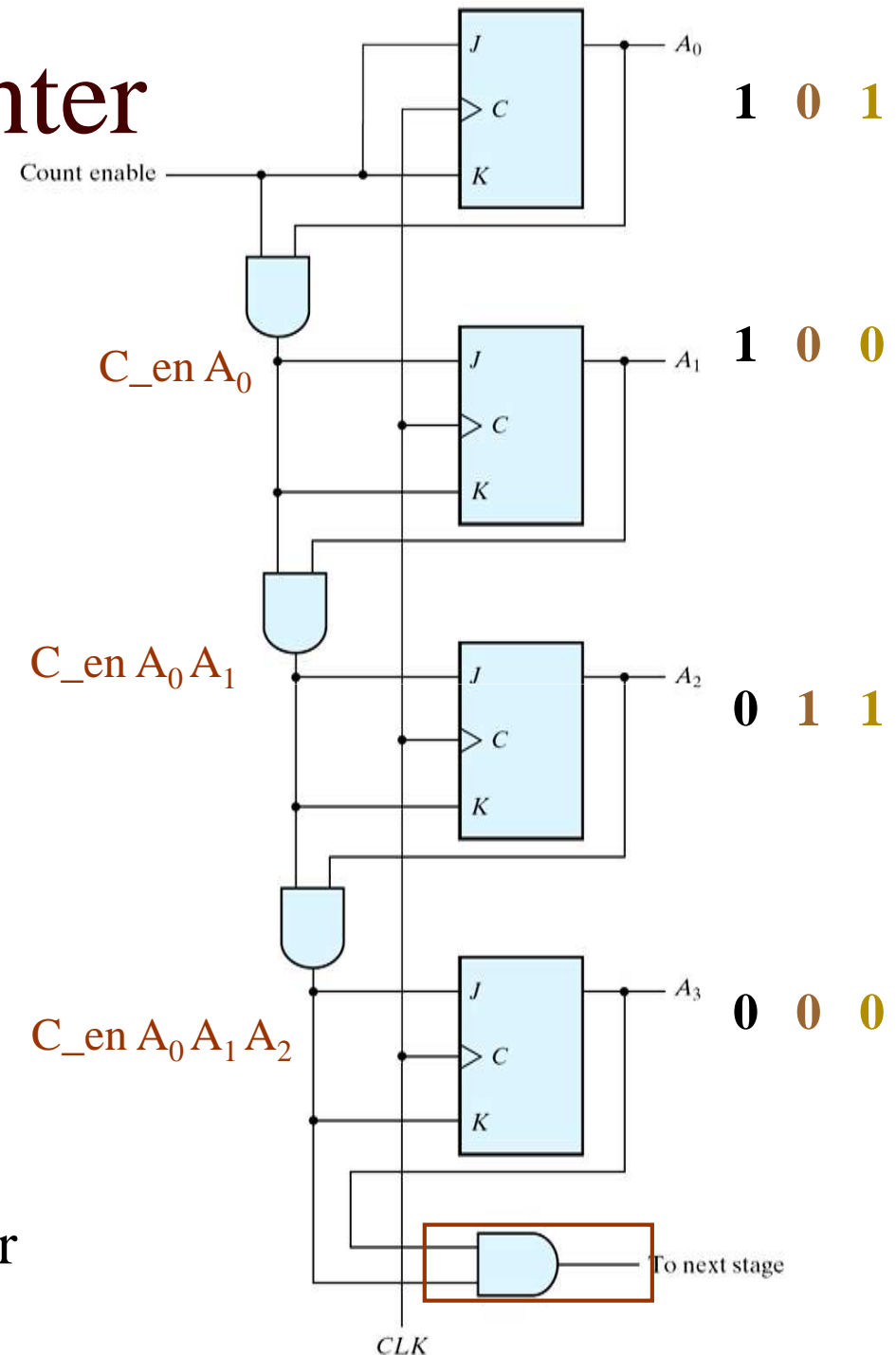


Design of a counter

Design of a synchronous 2 bit up/down counter using D flip flops

- ❑ Determine the number of flip-flops
- ❑ Draw state diagram
- ❑ Get excitation table
- ❑ Obtain the minimal expressions for inputs using K-map
- ❑ Draw the logic diagram from the expression.

The complete state diagram and table

 

Present State		Inputs X	Next State	
Q ₁	Q ₀		Q ₁	Q ₀
0	0	0	0	1
0	0	1	1	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	0
1	1	1	1	0

D flip-flop inputs

- If we use D flip-flops, then the D inputs will just be the same as the desired next states.
- Equations for the D flip-flop inputs are shown at the right.

Present State		Inputs	Next State		Excitation IP	
Q_1	Q_0	X	Q_1	Q_0	D1	D0
0	0	0	0	1	0	1
0	0	1	1	1	1	1
0	1	0	1	0	1	0
0	1	1	0	0	0	0
1	0	0	1	1	1	1
1	0	1	0	1	0	1
1	1	0	0	0	0	0
1	1	1	1	0	1	0

$$D_1 = Q_1 \oplus Q_0 \oplus X$$

$$D_0 = Q_0'$$

Flip-Flop Excitation Tables

Excitation Table:- the excitation table specifies the values for the flip-flop input signals needed to cause the transitions in the transition table.

Present State	Next State	F.F. Input
$Q(t)$	$Q(t+1)$	D
0	0	0
0	1	1
1	0	0
1	1	1

Present State	Next State	F.F. Input	
$Q(t)$	$Q(t+1)$	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

0 0 (No change)

0 1 (Reset)

1 0 (Set)

1 1 (Toggle)

0 1 (Reset)

1 1 (Toggle)


0 0 (No change)

1 0 (Set)

Design of a synchronous 3 bit up/down counter using JK flip flops

- ❑ Determine the number of flip-flops
- ❑ Draw state diagram
- ❑ Get excitaion table
- ❑ Obtain the minimal expressions for inputs
- ❑ Draw the logic diagram

□ State diagram

 

Excitation table

Present state			Mo de	Next state			Required inputs					
Q ₃	Q ₂	Q ₁	M	Q ₃	Q ₂	Q ₁	J ₃	K ₃	J ₂	K ₂	J ₁	K ₁
0	0	0	0	1	1	1	1	X	1	X	1	X
0	0	0	1	0	0	1	0	X	0	X	1	X
0	0	1	0	0	0	0	0	X	0	X	X	1
0	0	1	1	0	1	0	0	X	1	X	X	1
0	1	0	0	0	0	1	0	X	X	1	1	X
0	1	0	1	0	1	1	0	X	X	0	1	X
0	1	1	0	0	1	0	0	X	X	0	X	1
0	1	1	1	1	0	0	1	X	X	1	X	1
1	0	0	0	0	1	1	X	1	1	X	1	X
1	0	0	1	1	0	1	X	0	0	X	1	X
1	0	1	0	1	0	0	X	0	0	X	X	1
1	0	1	1	1	1	0	X	0	1	X	X	1
1	1	0	0	1	0	1	X	0	X	1	1	X
1	1	0	1	1	1	1	X	0	X	0	1	X
1	1	1	0	1	1	0	X	0	X	0	X	1
1	1	1	1	0	0	0	X	1	X	1	X	1

* PS=Present state *NS= Next state

Present State	Next State	F.F. Input	
$Q(t)$	$Q(t+1)$	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

$Q_3(PS)Q_3(NS) = 01$ then from excitation table of JK flip flop J_3K_3 should be $1X$ ($J_3=1$ $K_3=X$)

$Q_2(PS)Q_2(NS) = 01$ then from excitation table of JK flip flop J_2K_2 should be $1X$ ($J_2=1$ $K_2=X$)

Similarly fill all the rows of excitation inputs for all states of counter

K-maps for excitations of synchronous 3 bit U/D counter

	Q1M			
Q3Q2	1			
			1	
	X	X	X	X
	X	X	X	X

$$J3=Q2'Q1'M'+Q2Q1M$$

	Q1M			
Q3Q2	1		1	
	X	X	X	X
	X	X	X	X
	1		1	

$$J2=Q1'M'+Q1M$$

$$J1=1$$

	Q1M			
Q3Q2	X	X	X	X
	X	X	X	X
			1	
	1			

$$K3=Q2'Q1'M'+Q2Q1M$$

	Q1M			
Q3Q2	X	X	X	X
	1		1	
	1		1	
	X	X	X	X

$$K2=Q1'M'+Q1M$$

$$k1=1$$

Draw the final circuit of 3bit UP/DOWN counter using JK flip flop

□ Work for you