

# **Digital Electronics and Microprocessors**

Class 16

CHHAYADEVI BHAMARE

# MSI logic circuits(Chapter 9 of T1)

- Digital systems obtain data and information continuously operated on in some manner:
  - *Decoding/encoding.*
  - *Multiplexing/demultiplexing,.*
  - *Comparison; Code conversion;*
- These and other operations have been facilitated by the availability of numerous ICs in the MSI (medium-scale-integration) category.


# Decoders

- Decoders are used when an output or a group of outputs is to be activated only on the occurrence of a specific combination of input levels.
  - Often provided by outputs of a counter or a register.
 
# Decoders

- A **decoder** accepts a set of inputs that represents a binary number—activating only the output that corresponds to the input number.


For each of these input combinations, only one of the  $M$  outputs will be active (HIGH); all the other outputs are LOW.




Many decoders are designed to produce active-LOW outputs, where only the selected output is LOW while all others are HIGH.

# Decoders

## □ “*Enable*” Control

 


| $E$ | $I_1$ | $I_0$ | $Y_3$ | $Y_2$ | $Y_1$ | $Y_0$ |
|-----|-------|-------|-------|-------|-------|-------|
| 0   | x     | x     | 0     | 0     | 0     | 0     |
| 1   | 0     | 0     | 0     | 0     | 0     | 1     |
| 1   | 0     | 1     | 0     | 0     | 1     | 0     |
| 1   | 1     | 0     | 0     | 1     | 0     | 0     |
| 1   | 1     | 1     | 1     | 0     | 0     | 0     |

 

# Decoders

## □ Expansion

| $I_2 I_1 I_0$ | $Y_7 Y_6 Y_5 Y_4 Y_3 Y_2 Y_1 Y_0$ |
|---------------|-----------------------------------|
| 0 0 0         | 0 0 0 0 0 0 0 1                   |
| 0 0 1         | 0 0 0 0 0 0 1 0                   |
| 0 1 0         | 0 0 0 0 0 1 0 0                   |
| 0 1 1         | 0 0 0 0 1 0 0 0                   |
| 1 0 0         | 0 0 0 1 0 0 0 0                   |
| 1 0 1         | 0 0 1 0 0 0 0 0                   |
| 1 1 0         | 0 1 0 0 0 0 0 0                   |
| 1 1 1         | 1 0 0 0 0 0 0 0                   |



 


# Decoders

□ Active-High / Active-Low

| $I_1$ | $I_0$ | $Y_3$ | $Y_2$ | $Y_1$ | $Y_0$ |
|-------|-------|-------|-------|-------|-------|
| 0     | 0     | 0     | 0     | 0     | 1     |
| 0     | 1     | 0     | 0     | 1     | 0     |
| 1     | 0     | 0     | 1     | 0     | 0     |
| 1     | 1     | 1     | 0     | 0     | 0     |

| $I_1$ | $I_0$ | $Y_3$ | $Y_2$ | $Y_1$ | $Y_0$ |
|-------|-------|-------|-------|-------|-------|
| 0     | 0     | 1     | 1     | 1     | 0     |
| 0     | 1     | 1     | 1     | 0     | 1     |
| 1     | 0     | 1     | 0     | 1     | 1     |
| 1     | 1     | 0     | 1     | 1     | 1     |

   


# Implementation Using Decoders

- ❑ Each output is a minterm
- ❑ All minterms are produced
- ❑ Sum the required minterms

Example: Full Adder



$$S(x, y, z) = \sum(1, 2, 4, 7)$$

$$C(x, y, z) = \sum(3, 5, 6, 7)$$

 





# Implementation Using Decoders

  

# Seven-Segment Decoder

| <i>w x y z</i> | <i>a b c d e f g</i> |
|----------------|----------------------|
| 0 0 0 0        | 1 1 1 1 1 1 0        |
| 0 0 0 1        | 0 1 1 0 0 0 0        |
| 0 0 1 0        | 1 1 0 1 1 0 1        |
| 0 0 1 1        | 1 1 1 1 0 0 1        |
| 0 1 0 0        | 0 1 1 0 0 1 1        |
| 0 1 0 1        | 1 0 1 1 0 1 1        |
| 0 1 1 0        | 1 0 1 1 1 1 1        |
| 0 1 1 1        | 1 1 1 0 0 0 0        |
| 1 0 0 0        | 1 1 1 1 1 1 1        |
| 1 0 0 1        | 1 1 1 1 0 1 1        |
| 1 0 1 0        | x x x x x x x        |
| 1 0 1 1        | x x x x x x x        |
| 1 1 0 0        | x x x x x x x        |
| 1 1 0 1        | x x x x x x x        |
| 1 1 1 0        | x x x x x x x        |
| 1 1 1 1        | x x x x x x x        |

  


$$a = w + y + xz + x'z'$$

$$b = \dots$$

$$c = \dots$$

$$d = \dots$$

 

# Encoders

- ❑ Most decoders accept an input code & produce a HIGH (or LOW) at *one* and *only one* output line.
- A decoder identifies, recognizes, or detects a particular code.

# Encoders


- The opposite of decoding process is **encoding**.
- Performed by a logic circuit called an **encoder**.

An encoder has a number of input lines, only **one** of which is activated at a given time.

Shown is an encoder with  $M$  inputs and  $N$  outputs.


Inputs are active-HIGH, which means that they are normally LOW.

 It produces an  $N$ -bit output code, depending on which input is activated.


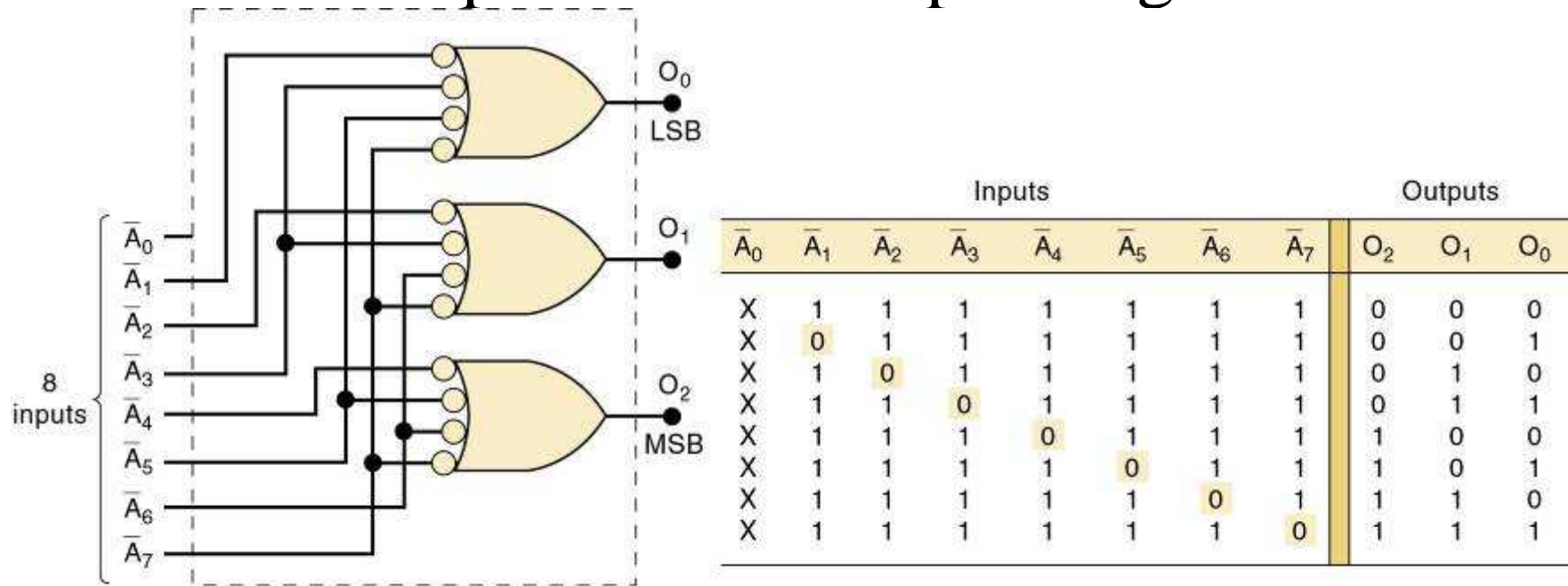
# Encoders

- An *octal-to-binary encoder* (8-line-to-3-line encoder) accepts eight input lines, producing a three-bit output code corresponding to the



\*Only one LOW input at a time

Logic circuit for an octal-to-binary (8-line-to-3-line) encoder.  
Only one input should be active at one time.

# Encoders



## ❑ Octal-to-Binary Encoder (8-to-3)

| $I_7$ | $I_6$ | $I_5$ | $I_4$ | $I_3$ | $I_2$ | $I_1$ | $I_0$ | $Y_2$ | $Y_1$ | $Y_0$ |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| 0     | 0     | 0     | 0     | 0     | 0     | 0     | 1     | 0     | 0     | 0     |
| 0     | 0     | 0     | 0     | 0     | 0     | 1     | 0     | 0     | 0     | 1     |
| 0     | 0     | 0     | 0     | 0     | 1     | 0     | 0     | 0     | 1     | 0     |
| 0     | 0     | 0     | 0     | 1     | 0     | 0     | 0     | 0     | 1     | 1     |
| 0     | 0     | 0     | 1     | 0     | 0     | 0     | 0     | 1     | 0     | 0     |
| 0     | 0     | 1     | 0     | 0     | 0     | 0     | 0     | 1     | 0     | 1     |
| 0     | 1     | 0     | 0     | 0     | 0     | 0     | 0     | 1     | 1     | 0     |
| 1     | 0     | 0     | 0     | 0     | 0     | 0     | 0     | 1     | 1     | 1     |

$$Y_2 = I_7 + I_6 + I_5 + I_4$$

$$Y_1 = I_7 + I_6 + I_3 + I_2$$

$$Y_0 = I_7 + I_5 + I_3 + I_1$$

  


# Priority Encoder

- A priority encoder is an encoder circuit that includes priority function.
- It means if two or more inputs are equal to 1 at the same time, the input having higher subscript number, considered as a higher priority. For example if D3 is 1 regardless of the value of the other input lines the result of output is 3 which is 11.
- If all inputs are 0, there is no valid input. For detecting this situation we considered a third output named V. V is equal to 0 when all input are 0 and is one for rest of the situations of TT.

# Priority Encoders

## □ 4-Input Priority Encoder



| $I_3$ | $I_2$ | $I_1$ | $I_0$ | $Y_1$ | $Y_0$ | $V$ |
|-------|-------|-------|-------|-------|-------|-----|
| 0     | 0     | 0     | 0     | 0     | 0     | 0   |
| 0     | 0     | 0     | 1     | 0     | 0     | 1   |
| 0     | 0     | 1     | x     | 0     | 1     | 1   |
| 0     | 1     | x     | x     | 1     | 0     | 1   |
| 1     | x     | x     | x     | 1     | 1     | 1   |

 

$$Y_1 = I_3 + I_2$$

$$Y_0 = I_3 + \bar{I}_2 I_1$$


$$V = I_3 + I_2 + I_1 + I_0$$

  


 
# Encoders

- A **priority encoder** ensures that when two or more inputs are activated, the output code will correspond to the highest-numbered input.



It has nine active-LOW inputs represent decimal digits 1 through 9, producing *inverted* BCD code corresponding to the highest-numbered activated input.

# Can u implement logic function using Encoders?

- Work for you

# Encoders

- A **switch encoder** can be used when BCD data must be entered manually into a digital system.
  - The 10 switches might be the keyboard switches on a calculator—representing digits 0 through 9.


# Encoders

The switches are of the normally open type, so the encoder inputs are all normally HIGH.


BCD output is 0000.

When a key is depressed, the circuit will produce the BCD code for that digit.

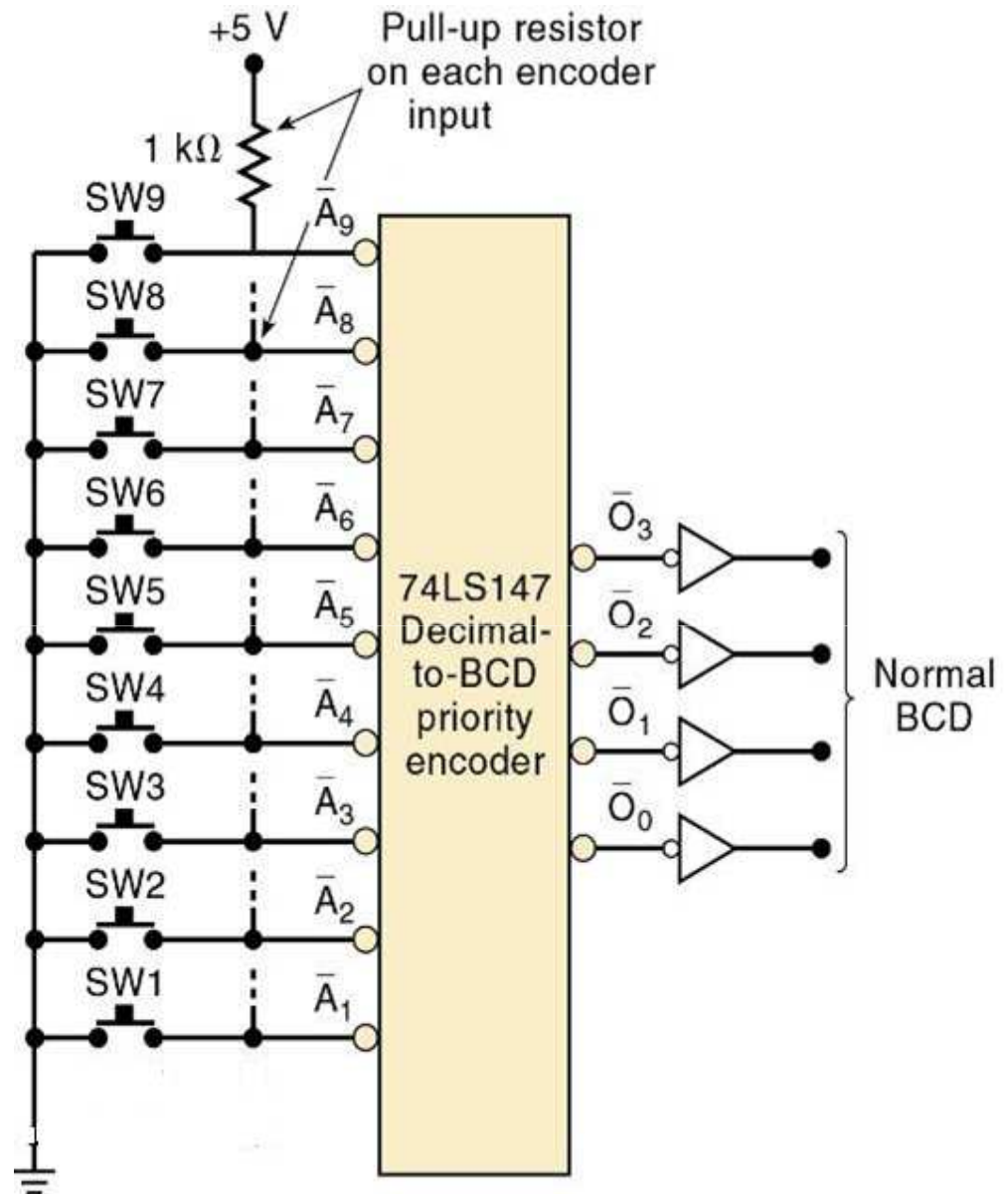
The 74LS147 is a *priority* encoder, so simultaneous key depressions produce the BCD code for the *higher-numbered* key.



# Multiplexers


 


| $S_1$ | $S_0$ | $Y$   |
|-------|-------|-------|
| 0     | 0     | $I_0$ |
| 0     | 1     | $I_1$ |
| 1     | 0     | $I_2$ |
| 1     | 1     | $I_3$ |


 


# Multiplexers

## □ 2-to-1 MUX

 
 


## □ 4-to-1 MUX

  



# Multiplexers

## □ Quad 2-to-1 MUX

 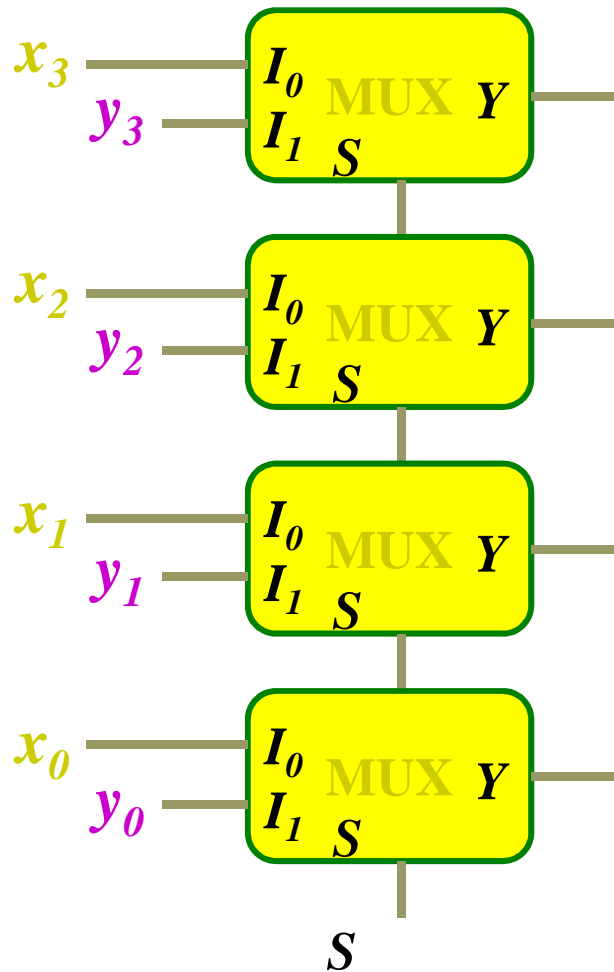

# Multiplexers

## □ Quad 2-to-1 MUX

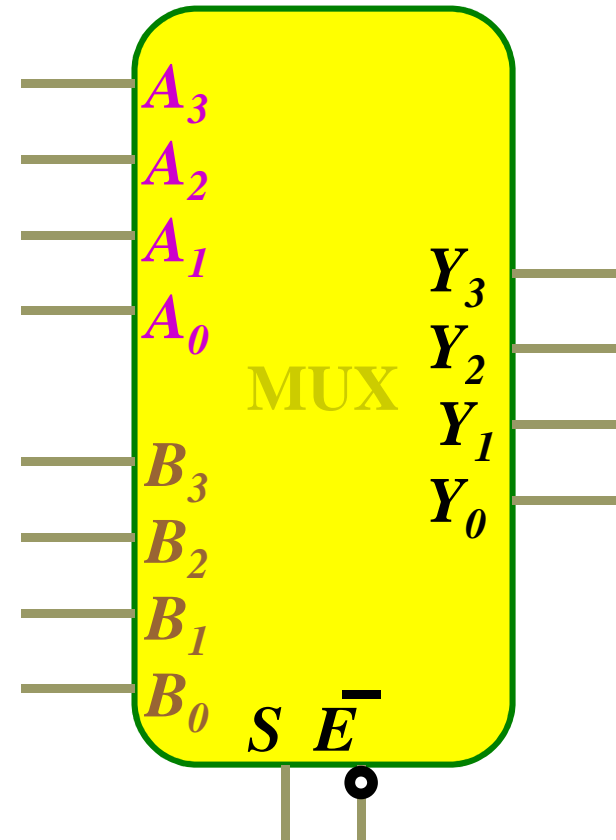 




# Function Implementation Using Multiplexers

## □ Example

$$F(x, y) = \sum(0, 1, 3)$$

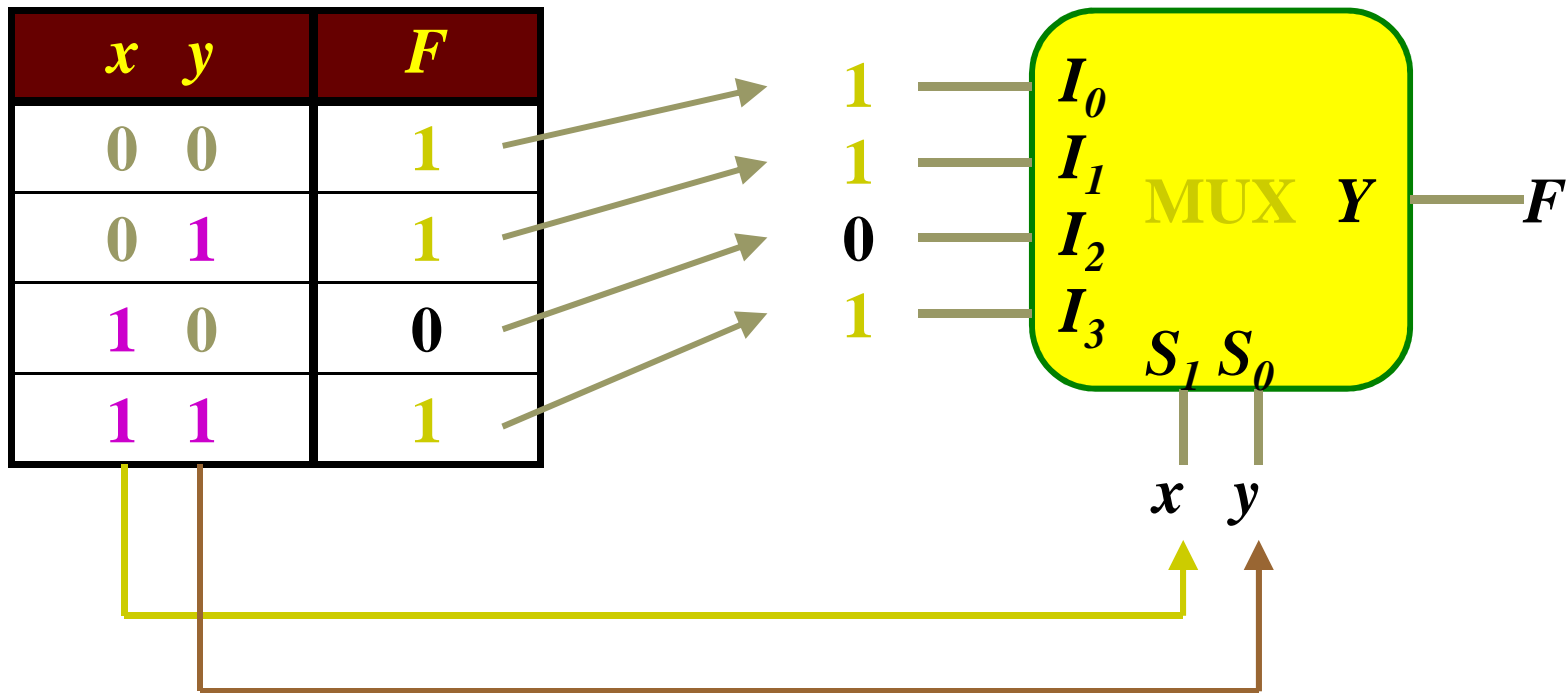


# Implementation Using Multiplexers

## □ Example

$$F(x, y, z) = \sum(1, 2, 6, 7)$$

| <i>x</i> | <i>y</i> | <i>z</i> | <i>F</i> |
|----------|----------|----------|----------|
| 0        | 0        | 0        | 0        |
| 0        | 0        | 1        | 1        |
| 0        | 1        | 0        | 1        |
| 0        | 1        | 1        | 0        |
| 1        | 0        | 0        | 0        |
| 1        | 0        | 1        | 0        |
| 1        | 1        | 0        | 1        |
| 1        | 1        | 1        | 1        |

 

# Implementation Using Multiplexers

## □ Example

$$F(x, y, z) = \sum(1, 2, 6, 7)$$


| $x$ | $y$ | $z$ | $F$ |
|-----|-----|-----|-----|
| 0   | 0   | 0   | 0   |
| 0   | 0   | 1   | 1   |
| 0   | 1   | 0   | 1   |
| 0   | 1   | 1   | 0   |
| 1   | 0   | 0   | 0   |
| 1   | 0   | 1   | 0   |
| 1   | 1   | 0   | 1   |
| 1   | 1   | 1   | 1   |

Group 1 (Rows 1-2):  $F = z$

Group 2 (Rows 3-4):  $F = \bar{z}$


Group 3 (Rows 5-6):  $F = 0$

Group 4 (Rows 7-8):  $F = 1$

 


Consider the following truth table that describes a function of 4 Boolean variables.

| A | B | C | D | F |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |

 

## Implementing the above function using 8:1 Mux

| A | B | C | D | F   |
|---|---|---|---|-----|
| 0 | 0 | 0 | 0 | 0   |
| 0 | 0 | 0 | 1 | 0   |
| 0 | 0 | 1 | 0 | 1   |
| 0 | 0 | 1 | 1 | 1   |
| 0 | 1 | 0 | 0 | $D$ |
| 0 | 1 | 0 | 1 | 1   |
| 0 | 1 | 1 | 0 | $D$ |
| 0 | 1 | 1 | 1 | 1   |
| 1 | 0 | 0 | 0 | 0   |
| 1 | 0 | 0 | 1 | 0   |
| 1 | 0 | 1 | 0 | 1   |
| 1 | 0 | 1 | 1 | 1   |
| 1 | 1 | 0 | 0 | 0   |
| 1 | 1 | 0 | 1 | 0   |
| 1 | 1 | 1 | 0 | $D$ |
| 1 | 1 | 1 | 1 | 1   |

 


# Implementation Using Multiplexers

## □ Example

$$F(A, B, C, D) = \sum(1, 3, 4, 11, 12, 13, 14, 15)$$


| A | B | C | D | F |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

$\left. \begin{array}{l} F = D \\ F = D \end{array} \right\} F = D$   
 $\left. \begin{array}{l} F = D \\ F = D \end{array} \right\} F = D$   
 $\left. \begin{array}{l} F = \bar{D} \\ F = \bar{D} \end{array} \right\} F = \bar{D}$   
 $\left. \begin{array}{l} F = 0 \\ F = 0 \end{array} \right\} F = 0$   
 $\left. \begin{array}{l} F = 0 \\ F = 0 \end{array} \right\} F = 0$   
 $\left. \begin{array}{l} F = D \\ F = D \end{array} \right\} F = D$   
 $\left. \begin{array}{l} F = 1 \\ F = 1 \end{array} \right\} F = 1$   
 $\left. \begin{array}{l} F = 1 \\ F = 1 \end{array} \right\} F = 1$



 


# Multiplexer Expansion

- 8-to-1 MUX using Dual 4-to-1 MUX

 

  
 
we can use the 4:1 multiplexer to implement these three operations, so it is functionally complete.





# Multiplexer Applications

## Parallel-to-serial converter.

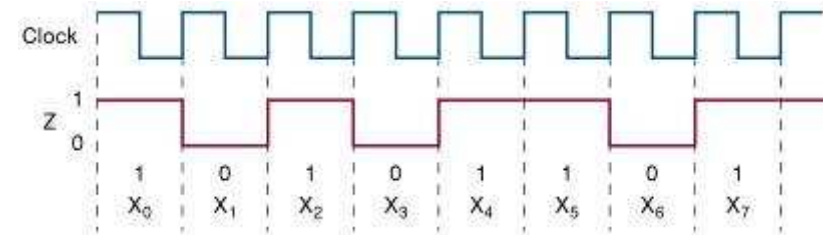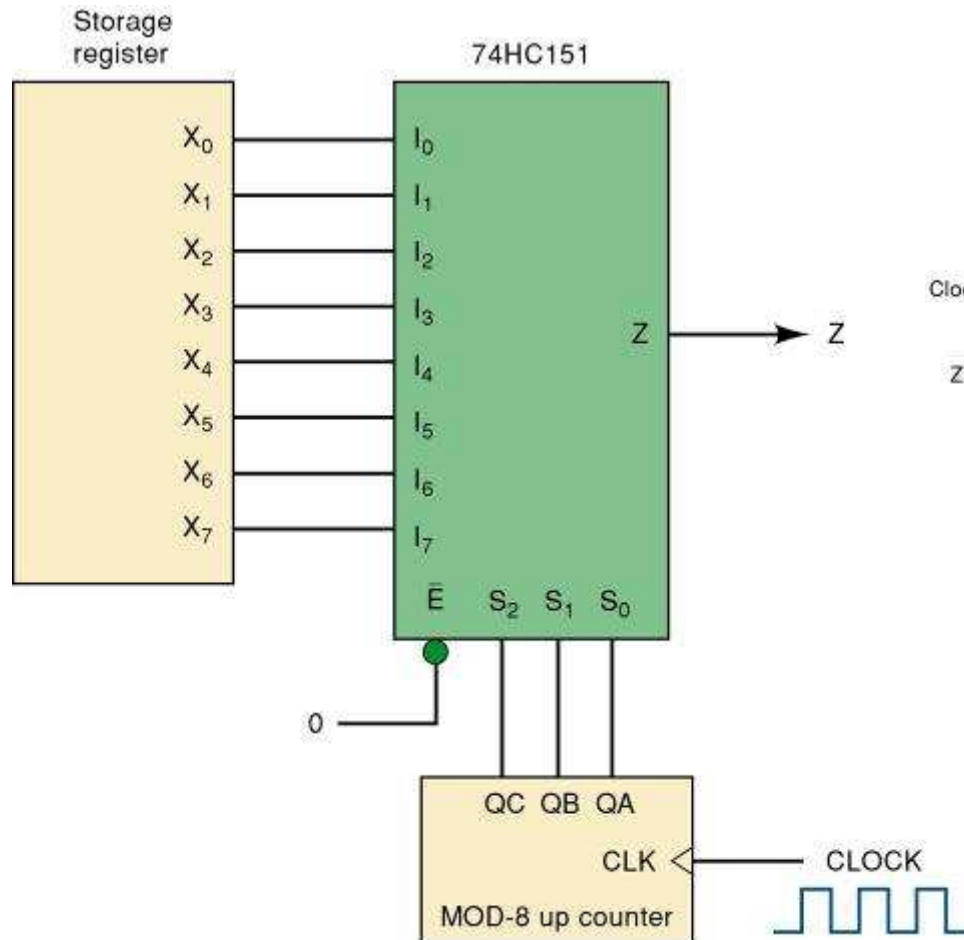

**Waveforms for  
 $X_7X_6X_5X_4X_3X_2X_1X_0$**

**10110101**

# Multiplexer Applications

**Multiplexer used to implement a logic function described by the truth table.**

