

# **Digital Electronics and Microprocessors**

---

Class 6

CHHAYADEVI BHAMARE




## Exclusive OR and Exclusive NOR Circuits

---

- ❑ The exclusive OR (XOR) produces a HIGH output whenever the two inputs are at opposite levels.
- ❑ The exclusive NOR (XNOR) produces a HIGH output whenever the two inputs are at the same level.
- ❑ XOR and XNOR outputs are opposite.

 (a) Exclusive-OR circuit and truth table; (b) traditional XOR gate symbol; (c) IEEE/ANSI symbol for XOR gate.



A	B	x
0	0	0
0	1	1
1	0	1
1	1	0



Quad XOR Chips

74LS86 Quad XOR(TTL family)


74C86 Quad XOR(CMOS family)

74HC86 Quad XOR( HS CMOS)


XOR gate symbols

  

 
(a) Exclusive-NOR circuit; (b) traditional symbol for XNOR gate; (c) IEEE/ANSI symbol.



XNOR gate symbols


 


(b)

 

(c)

# XOR Timing Diagram

  




# Basic Identities of XOR Operation:

---

- $X \oplus 0 = X$
- $X \oplus 1 = X'$
- $X \oplus X = 0$
- $X \oplus X' = 1$
- $X \oplus Y' = X' \oplus Y = (X \oplus Y)' = X \odot Y$

# Graphical presentation of important XOR/XNOR rules and gate equivalence.




---

 

**Example:**

Show that  $(A \odot B) \oplus (C \odot D) = A \oplus B \oplus C \oplus D$

---

   





# Applications of X-OR/X-NOR

---

- ❑ Odd function/Even function
- ❑ Even/Odd parity generator and checker
- ❑ Binary to gray/Gray to binary

# ODD Function:

---

As shown in the K-map,  $X \oplus Y \oplus Z = 1$ , IFF (if and only if) the number of 1's in the input combination is odd.


X	Y	Z	ODD
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$\begin{matrix} z \\ xy \end{matrix}$	$Z'$	$Z$
$X'Y'$	0	1
$X'Y$	1	0
$XY$	0	1
$XY'$	1	0

$$\text{ODD} = X \oplus Y \oplus Z$$

# Parity Generation and checking


---

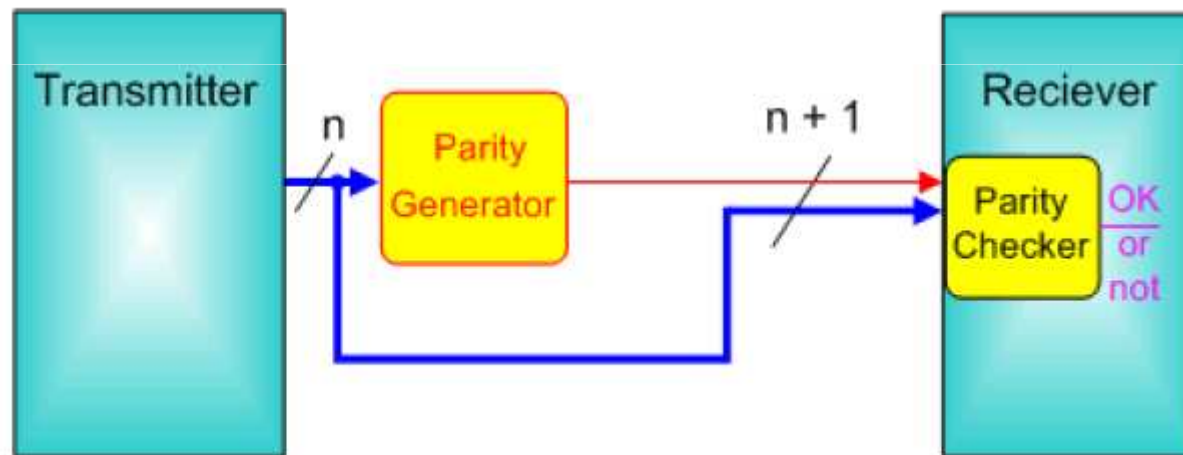

# Even Parity Generation (Odd Function)

X	Y	Z	P(E)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$\begin{array}{c} z \\ \hline xy \end{array}$	$Z'$	$Z$
$X'Y'$	0	1
$X'Y$	1	0
$XY$	0	1
$XY'$	1	0

 

$$P(E) = X \oplus Y \oplus Z$$

# Parity Generator and Checker


- XOR and XNOR gates are useful in circuits for parity generation and checking.

Even Parity Generator  
truth table




D3	D2	D1	D0	Parity
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0
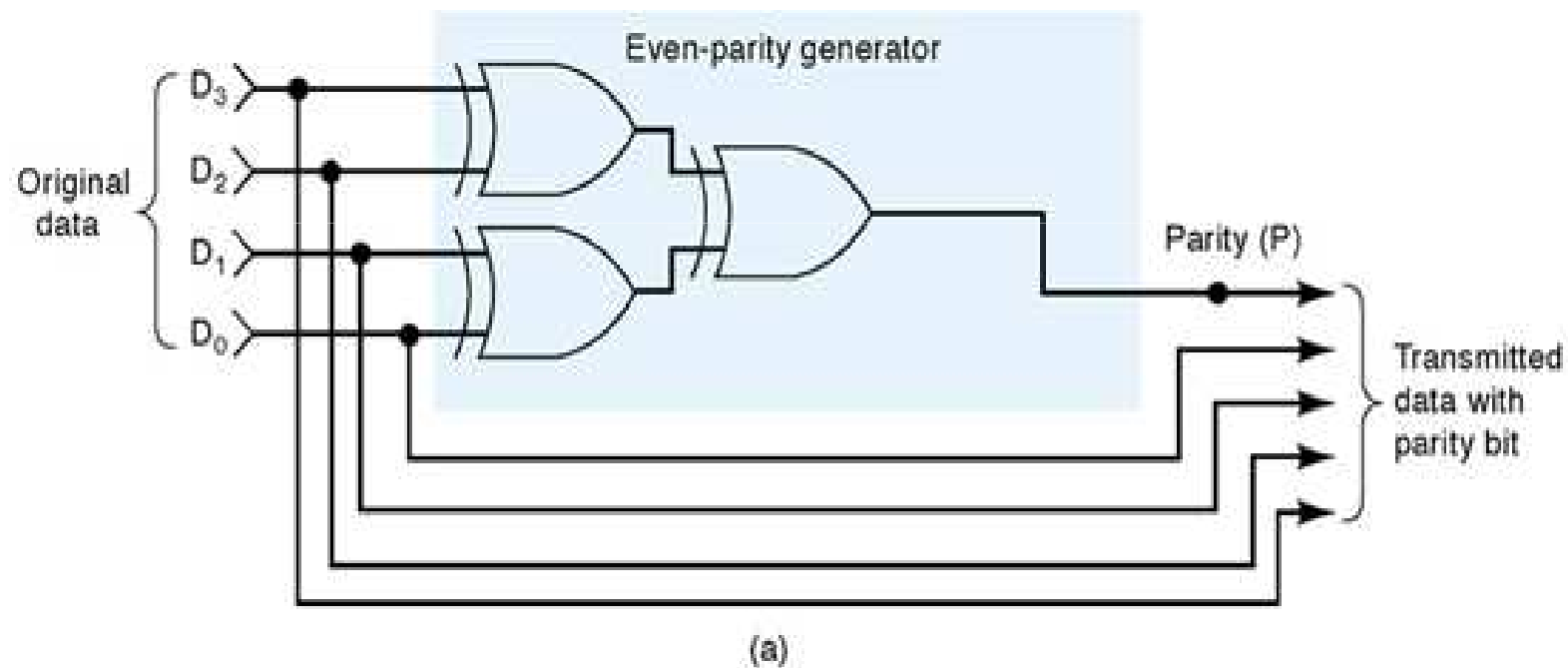
# Even Parity Generator Ckt for 4-bit data


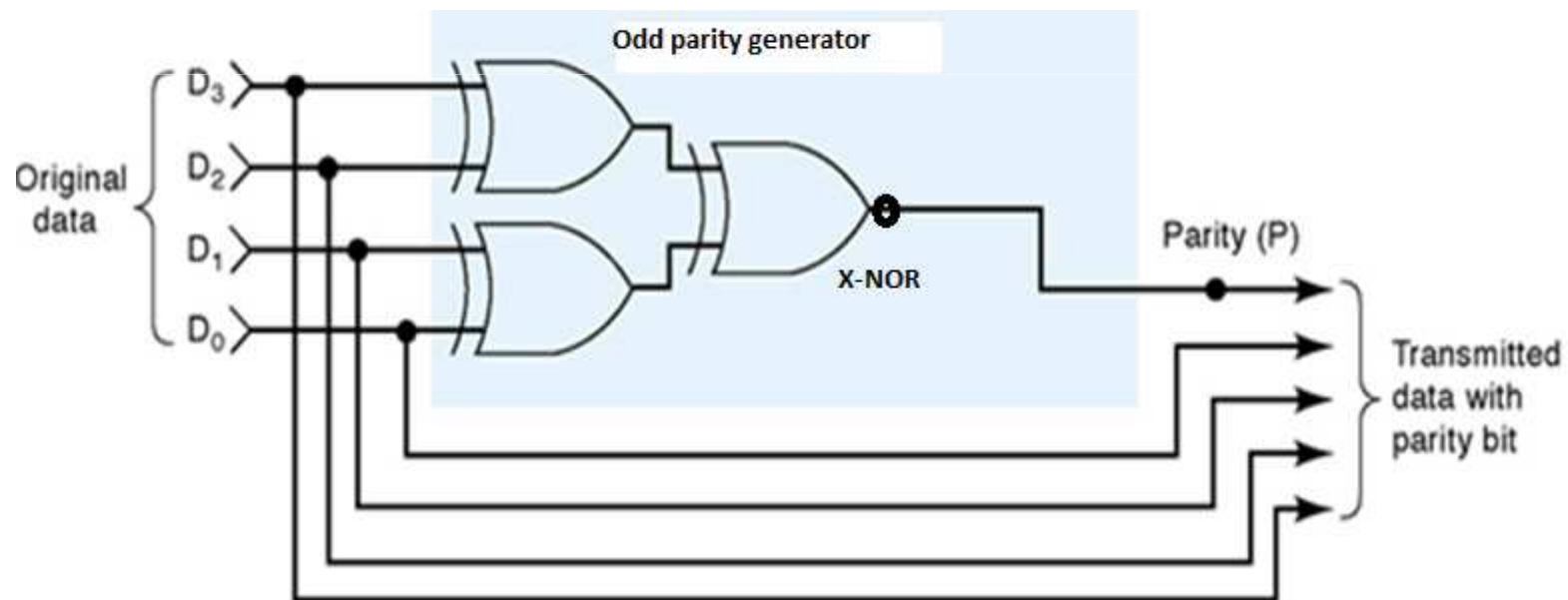
# Odd parity generation for 4 bit data


Add an inverter at the output of the previous(even parity generator ckt) ckt



## 3-bit even parity checker (4-input, 3 data inputs 1 parity input)

Four Bits Received				Parity Error Check
X	Y	Z	P	C
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

	$Z'P'$	$Z'P$	$ZP$	$ZP'$
$X'Y'$	0	1	0	1
$X'Y$	1	0	1	0
$XY$	0	1	0	1
$XY'$	1	0	1	0

 


C=0 (No Error)

C=1(Error)



## 3-bit parity generator/checker ckt


---

 

For Generator P input of this circuit should be zero always and output will be parity bit

For checker the P input is the parity bit Input and output will be checked output(error/no error)


# Enable/Disable Circuits

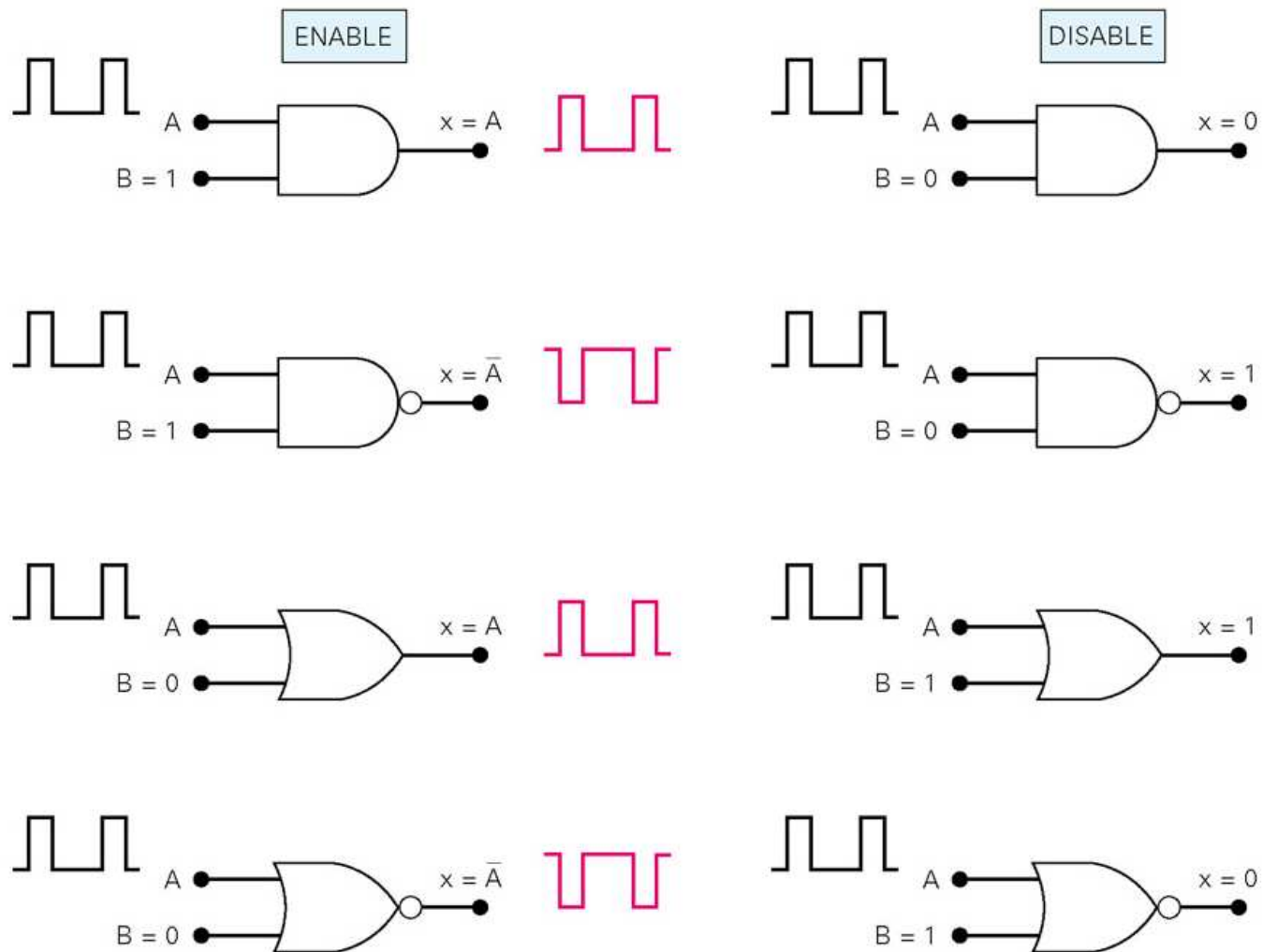

## Enable/Disable Circuits cont.

---

 **Example:-** Design a logic circuit that will allow a signal to pass to the output only when control inputs B and C are both HIGH; otherwise, the output will stay LOW.




Refer example 4-23 of T1

Example:- Design a logic circuit that controls the passage of the signal A according to the following requirements:

---

 1. Output X will equal A when control inputs B and C are same.
2. X will remain HIGH when B and C are Different

$X=A$  when  $B=C$  and  $X=1$  when B Not Equal to C





# Take home problems

---

4-2,4-3,4-5,4-7,4-8,4-16,4-22,4-25,4-38