

Digital Electronics and Microprocessors

Class 4

CHHAYADEVI BHAMARE



Alternate Logic-Gate Representations

- To convert a standard symbol to an alternate:
 - Invert each input and output (add an inversion bubble where there are none on the standard symbol, and remove bubbles where they exist on the standard symbol).
 - Change a standard OR gate to an AND gate, or an AND gate to an OR gate.



Alternate Logic-Gate Representations

- ❑ The equivalence can be applied to gates with any number of inputs.
- ❑ No standard symbols have bubbles on their inputs. All of the alternate symbols do.
- ❑ The standard and alternate symbols represent the same physical circuitry.



Alternate Logic-Gate Representations

- ❑ Active high – an input or output has no inversion bubble.
- ❑ Active low – an input or output has an inversion bubble.
- ❑ An AND gate will produce an active output when all inputs are in their active states.
- ❑ An OR gate will produce an active output when any input is in an active state.



Which Gate Representation to Use


- ❑ Using alternate and standard logic gate symbols together can make circuit operation clearer.
- ❑ When possible choose gate symbols so that bubble outputs are connected to bubble input and nonbubble outputs are connected to nonbubble inputs.



Which Gate Representation to Use

- ❑ When a logic signal is in the active state (high or low) it is said to be asserted.
- ❑ When a logic signal is in the inactive state (high or low) it is said to be unasserted.
- ❑ A bar over a signal means asserted (active) low.
- ❑ The absence of a bar over a signal means asserted (active) high.


Example

 

This circuit does not facilitate an understanding of how the circuit functions


A	B	C	D	Z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Example continued

 

Output Z will go high whenever either $A=B=1$ or $C=D=1$ (Or both)


Example continued

 

Output Z will go low only when A or B is low and C or D is low

 
Example

- when the output of the logic ckt in fig goes low it activates another logic ckt. Modify the ckt diagram to represent the circuit operation more effectively




Alternate gate representation

 - Because Z is to be active low, the symbol for OR gate 2 must be changed to its alternate symbol. The new OR gate2 symbol has bubble inputs, and so the AND gate and OR gate symbols must be changed to bubbled outputs.
- The inverter has already bubble output




 Example

- The logic ckt in fig is being used to activate an alarm when its output Z goes High. Modify the circuit diagram so that it represents the ckt operation more effectively.



Alternate logic ckt

 



Algebraic Simplification

- ❑ Place the expression in SOP form by applying DeMorgan's theorems and multiplying terms.
- ❑ Check the SOP form for common factors and perform factoring where possible.
- ❑ Note that this process may involve some trial and error to obtain the simplest result.



Designing Combinational Logic Circuits

- To solve any logic design problem:
 - Interpret the problem and set up its truth table.
 - Write the AND (product) term for each case where the output equals 1.
 - Combine the terms in SOP form.
 - Simplify the output expression if possible.
 - Implement the circuit for the final, simplified expression.

Example application:- Majority Circuit

A logic circuit having 3 inputs, A, B, C will have its output HIGH only when a majority of the inputs are HIGH.

Step 1 Set up the truth table

A	B	C	x
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

→ $\bar{A}BC$

→ $A\bar{B}C$

→ $AB\bar{C}$

→ ABC

Step 2 Write the AND term for
each case where the output
is a 1.



Step 3 Write the SOP form the output

$$X = \overline{A}BC + A\overline{B}C + AB\overline{C} + ABC$$

Step 4 Simplify the output expression (ref. p. 119 of T1)


$$X \equiv \overline{A}BC + A\overline{B}C + AB\overline{C} + ABC$$

$$X \equiv \overline{A}BC + ABC + A\overline{B}C + ABC + AB\overline{C} + ABC$$

$$\equiv BC(\overline{A} + A) + AC(\overline{B} + B) + AB(\overline{C} + C)$$

$$\equiv BC + AC + AB$$

Step 5 Implement the circuit

 



Karnaugh Map Method

- ❑ A graphical method of simplifying logic equations or truth tables. Also called a K map.
- ❑ Theoretically can be used for any number of input variables, but practically limited to 5 or 6 variables.
- ❑ K Map shows the relationship between inputs & outputs

Karnaugh Map Method

- The truth table values are placed in the K map as shown in the next page.
- Adjacent K map square differ in only one variable both horizontally and vertically. $\overline{A}\overline{B}, \overline{A}B, AB, A\overline{B}$
- A SOP expression can be obtained by ORing all squares that contain a 1.

A	B	X
0	0	1 → $\overline{A}\overline{B}$
0	1	0
1	0	0
1	1	1 → AB

$$\left\{ x = \overline{A}\overline{B} + AB \right\}$$

(a)

	\overline{B}	B
\overline{A}	1	0
A	0	1

Karnaugh maps and truth tables for three variables.

A	B	C	X
0	0	0	1 → $\bar{A}\bar{B}\bar{C}$
0	0	1	1 → $\bar{A}\bar{B}C$
0	1	0	1 → $\bar{A}B\bar{C}$
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1 → $AB\bar{C}$
1	1	1	0

$$\left\{ \begin{aligned} X = & \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C \\ & + \bar{A}B\bar{C} + AB\bar{C} \end{aligned} \right\}$$

(b)

	\bar{C}	C
$\bar{A}\bar{B}$	1	1
$\bar{A}B$	1	0
$A\bar{B}$	1	0
AB	0	0

Karnaugh maps and truth tables for four variables.

A	B	C	D	X	
0	0	0	0	0	
0	0	0	1	1	$\rightarrow \bar{A}\bar{B}\bar{C}D$
0	0	1	0	0	
0	0	1	1	0	
0	1	0	0	0	
0	1	0	1	1	$\rightarrow \bar{A}B\bar{C}D$
0	1	1	0	0	
0	1	1	1	0	
1	0	0	0	0	
1	0	0	1	0	
1	0	1	0	0	
1	0	1	1	0	
1	1	0	0	0	
1	1	0	1	1	$\rightarrow ABCD$
1	1	1	0	0	
1	1	1	1	1	$\rightarrow ABCD$

$$\left\{ \begin{array}{l} X = \bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}D \\ + A\bar{B}\bar{C}D + ABCD \end{array} \right\}$$

	$\bar{C}D$	$\bar{C}\bar{D}$	CD	$C\bar{D}$
$\bar{A}B$	0	1	0	0
$\bar{A}\bar{B}$	0	1	0	0
AB	0	1	1	0
$A\bar{B}$	0	0	0	0